


UNIVERSITY OF CALIFORNIA
Electrical Engineering and Computer Sciences

EECS 145L Electronic Transducer Lab
MIDTERM #2 (100 points maximum)

(closed book, calculators OK- note formulas on last page)
(You will not receive full credit if you do not show your work)

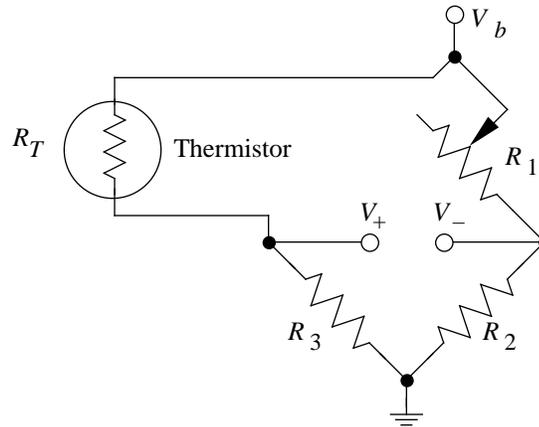PROBLEM 1 (45 points)

You wish to measure air temperatures over the range from 0°C to 50°C using the thermistor bridge shown below.



Assume the following:

- $R_2 = R_3 = 5 \text{ k} \Omega$
- You use an instrumentation amplifier with a gain of 5: $V_0 = 5 (V_+ - V_-)$.
- The thermistor resistance R_T vs. temperature T as shown in the table below

0°C	10°C	20°C	30°C	40°C	50°C
10.000 k	6.667 k	5.000 k	3.333 k	2.500 k	1.667 k

- $dR_T/dT = -150 \text{ } \Omega/\text{ }^\circ\text{C}$ at 20 °C.

You then perform a series of experiments to explore the thermistor self-heating of your system and to determine the best bias voltage V_b .

Experiment 1: With $V_b = 1$ volt and the thermistor in **water** at 20°C, you adjust R_1 to make the amplifier output $V_0 = 0.000$ volts. (Assume that there is no self heating in water with $V_b = 1$ volt)

- a. (4 points) What are the values of R_1 and R_T ?

- b. (4 points) What electrical power is consumed by the thermistor?

Experiment 2: You then move the thermistor to **air** at 20 °C, wait a while, and find that the amplifier output $V_0 = 0.0075$ volts ($V_b = 1$ volt).

- c. (5 points) What is the thermistor resistance R_T ?

- d. (4 points) What is the temperature of the thermistor?

- e. (4 points) What electrical power is consumed by the thermistor?

Experiment 3: With the thermistor in air at 20 °C, you increase V_b to 10 volts, wait a while, and find that the amplifier output $V_0 = 8.333$ volts.

- f. (5 points) What is the thermistor resistance R_T ?

- g. (4 points) What is the temperature of the thermistor?


- h. (4 points) What electrical power is consumed by the thermistor?

- i. (5 points) From your calculations of experiment 3, what is the thermal dissipation coefficient in mW per C°?

- j. (6 points) Comment on the design factors that determine the approximate **minimum** and **maximum** bias voltages of this application.

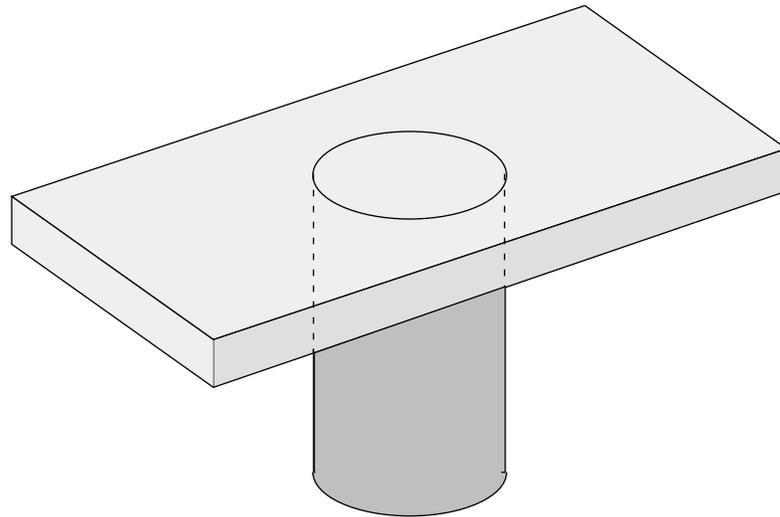PROBLEM 2 (45 points)

You are assigned the task of designing a truck scale for the North Dakota Department of Transportation. The scale consists of a large steel plate at the road level sitting on top of a large steel cylinder. When a truck drives onto the plate the steel cylinder is slightly compressed along its axis. The ambient temperature is expected to vary from -20°C to $+40^{\circ}\text{C}$. The thermal expansion coefficient of the steel cylinder is $10 \text{ ppm}/^{\circ}\text{C}$.



Design a system that meets the following requirements:

- The system should produce an output that is proportional to the weight of the truck.
- The maximum truck weight of 10,000 kg should produce an output of 10 volts.
- Trucks are to be weighed to an accuracy of 100 kg over the full temperature range.

Assume the following:

- You have decided to use four metal foil strain gauges with gauge factor $G_S = 2.00$ and an unstrained resistance of 100 Ω (similar to those used in the 145L lab)
- You may use any electronic components used in the 145L lab, but keep it simple.
- You cement the strain gauges (to wherever you decide to place them) at a temperature of 20°C . At this temperature, the strain is zero.

- The maximum truck weight of 10,000 kg produces a compressive strain $\Delta L/L = -0.2\%$
 - The steel cylinder is hollow so the load only compresses the steel cylinder along its length and changes in diameter are negligible.
 - All dimensions (e.g. length and diameter) change equally when the temperature changes.
 - The steel plate weighs 1,000 kg.
 - The resistivity of the strain gauge metal foil does not depend on temperature.
- a. (20 points) Sketch your circuit, showing all essential components. **Also**, sketch the placement and orientation of the four strain gauges on the previous drawing.

- c. (5 points) With no load on the scale, what are the resistances of the 4 strain gauges and the voltages at 3 key points in your circuit (2 bridge outputs, 1 amplifier output) at $+20^\circ\text{C}$?

Equations, some of which you may need:

$$R(T) = R(T_0) \exp\left(\frac{1}{T} - \frac{1}{T_0}\right) \quad V_{\text{rms}} = \sqrt{B[(D_1 G)^2 + (D_0)^2]}$$

$$V(t) = V_0 \sin(\omega t) \quad \omega = 2\pi f \quad V_0 = A(V_+ - V_-)$$

$$|G| = \frac{1}{\sqrt{1 + (f/f_c)^{2n}}} \quad \tan \frac{\phi}{n} = \frac{f}{f_c} \quad N(x) = N(0)e^{-x^2}$$

$$x = e^{-\alpha t} [A \cos(\omega t) + B \sin(\omega t)] = Re^{-\alpha t} \cos(\omega t + \phi) \quad V = q/C$$

$$v = v_0 + at \quad x = x_0 + v_0 t + 0.5 at^2 \quad (\text{constant } a) \quad g = 10 \text{ m s}^{-2}$$

$$T = T_2 - (T_2 - T_1)e^{-t/\tau} \quad I = I_0 e^{-kLC} \quad x = \frac{V}{dV/dx}$$

$$I_{\text{rms}} = \sqrt{2qI(F_2 - F_1)} \quad q = 1.60 \times 10^{-19} \text{ Coulombs}$$

$$V_{\text{rms}} = \sqrt{4kTR(F_2 - F_1)} \quad k = 1.38 \times 10^{-23} \text{ Volt}^2 \text{ sec ohm}^{-1} \text{ }^\circ\text{K}^{-1}$$

$$R_T = R_3 \frac{V_b R_1 - V_0(R_1 + R_2)}{V_b R_2 + V_0(R_1 + R_2)} \quad V_0 = G_\pm(V_+ - V_-) + G_c(V_+ + V_-)$$

$$f_c = \frac{1}{2RC} \quad \text{“CMRR”} = \frac{G_\pm}{G_c} \quad \text{“CMR”} = 20 \log_{10} \frac{G_\pm}{G_c}$$

$$R = A/L \quad \frac{R}{L} = G_s \quad \frac{L}{R} = V_0 = V_b G_s \quad \frac{L}{R}$$

$$V_T = V_{\text{BE2}} - V_{\text{BE1}} = \frac{kT}{q} \ln \frac{I_1}{I_2} \quad k/q = 86.17 \mu\text{V/K}$$

$$P_R = AT^4 = 5.6696 \times 10^{-8} \text{ W m}^{-2} \text{ K}^4$$

$$E = hc/\lambda \quad hc = 1240 \text{ eV nm} \quad \lambda_{\text{max}} = (2.8978 \times 10^6 \text{ nm K})/T$$

$$= \frac{T_{n+2} - T_{n+1}}{T_{n+1} - T_n} \quad T_{\text{equ}} = T_{n+1} + \frac{T_{n+2} - T_{n+1}}{1 - \dots}$$

$$Q = I + I^2 R/2 + K_p(T_s - T_0) + K_a(T_a - T_0) \quad T_{\text{equ}} = \frac{I + I^2 R/2 + K_p T_s + K_a T_a}{K_p + K_a}$$

$$\mu \quad \bar{a} = \frac{1}{m} \sum_{i=1}^m a_i \quad \sigma_a = \frac{1}{m-1} \sum_{i=1}^m (a_i - \bar{a})^2 \quad \bar{a} = \frac{a}{\sqrt{m}}$$

$$f = \sqrt{\frac{f_1^2}{a_1^2} + \frac{f_2^2}{a_2^2} + \dots + \frac{f_n^2}{a_n^2}}$$

Johnson noise = 129 μV for 1 MHz and 1 M

Iron+Constantan - 52.6 $\mu\text{V}/^\circ\text{C}$ W+W(Rh) - 16.0 $\mu\text{V}/^\circ\text{C}$