

EECS 40, Spring 2007
Prof. Chang-Hasnain
Test #2

October 8, 2007
 Total Time Allotted: 50 minutes
 Total Points: 100

1. This is a closed book exam. However, you are allowed to bring one page (8.5" x 11"), single-sided notes.
2. No electronic devices, i.e. calculators, cell phones, computers, etc.
3. SHOW all the steps on the exam. Answers without steps will be given only a small percentage of credits. Partial credits will be given if you have proper steps but no final answers.
4. Draw BOXES around your final answers.
5. **Remember to put down units. 1 point will be taken off per missed unit.**

Last (Family) Name: _____

First Name: _____

Student ID: _____ **LAB Session**: _____

Signature: _____

Score:	
Problem 1 (16 pts)	
Problem 2 (28 pts):	
Problem 3 (56 pts):	
Total	

1. (16 pts) Phasors and complex numbers

a) (6 pts) Convert $\vec{V} = \mathbf{V}$ to phasor notation. **Both polar and exponential form are acceptable.**

$$\vec{V} = \frac{4\sqrt{2} - j8}{2 - j2\sqrt{2}} = \frac{4\sqrt{2}(1 - j\sqrt{2})}{2(1 - j\sqrt{2})} = 2\sqrt{2} \angle 0 \text{ V (pink)}$$

$$\vec{V} = \frac{4\sqrt{2} + j8}{2 + j2\sqrt{2}} = \frac{4\sqrt{2}(1 + j\sqrt{2})}{2(1 + j\sqrt{2})} = 2\sqrt{2} \angle 0 \text{ V (white)}$$

$$\vec{V} = \frac{4\sqrt{2} - j8}{2 - j2\sqrt{2}} = \frac{4\sqrt{2}(1 - \sqrt{2})}{2(1 - j\sqrt{2})} = 2\sqrt{2} \angle 0 \text{ V (yellow)}$$

b) (3 pts) What is $v(t)$, in **cosinusoidal** form? Assume frequency is ω .

$$v(t) = 2\sqrt{2} \cos(\omega t) \text{ V (all)}$$

c) (4 pts) Convert $\vec{V}_2 = \mathbf{V}$ to phasor notation. **Both polar and exponential form are acceptable.**

$$\vec{V}_2 = j = e^{j\frac{\pi}{2}} = 1 \angle 90 \text{ V (yellow and pink)}$$

$$\vec{V}_2 = -j = e^{-j\frac{\pi}{2}} = 1 \angle -90 \text{ V (white)}$$

d) (3 pts) What is $v_2(t)$, in **cosinusoidal** form? Assume frequency is ω .


$$v_2(t) = \cos(\omega t + \frac{\pi}{2}) \text{ V (yellow and pink)}$$

$$v_2(t) = \cos(\omega t - \frac{\pi}{2}) \text{ V (white)}$$

2. (28 pts) Complex impedance.

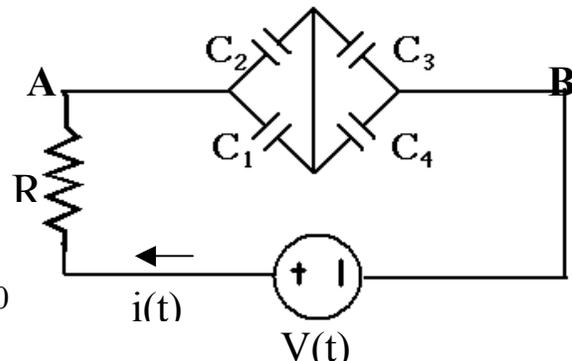a) (8 pts) $C_1=C_2=C_3=C_4=\mu\text{F}$, $R= \text{Ohm}$ $V(t)=10\cos(2\pi ft)$ V, frequency $f = \frac{10^6}{2\pi}$ Hz

What is the equivalent impedance \overline{Z}_{AB} ?



$$C_{eq} = (C_1 + C_2) \parallel (C_3 + C_4) = (2\mu\text{F}) \parallel (2\mu\text{F}) = 1\mu\text{F}$$

(yellow)

$$\overline{Z}_{AB} = \frac{1}{j\omega C} = \frac{1}{j(10^6 \text{ rads/s})(10^{-6} \text{ F})} = \frac{1}{j} \Omega = 1\angle -90$$

(yellow)

$$C_{eq} = (C_1 + C_2) \parallel (C_3 + C_4) = (4\mu\text{F}) \parallel (4\mu\text{F}) = 2\mu\text{F} \text{ (white and pink)}$$

$$\overline{Z}_{AB} = \frac{1}{j\omega C} = \frac{1}{j(10^6 \text{ rads/s})(2 \times 10^{-6} \text{ F})} = \frac{1}{2j} \Omega = -\frac{j}{2} \Omega \text{ (white and pink)}$$

b) (6 pts) What is the current $i(t)$ in phasor form?

$$\overline{Z}_{eq} = R + C_{eq} = 1 + \frac{1}{j} \Omega = 1 - j\Omega = \sqrt{2}\angle -45^\circ \text{ (yellow)}$$

$$\overline{Z}_{eq} = R + C_{eq} = 2 + \frac{1}{2j} \Omega = 2 - \frac{j}{2} \Omega = \frac{\sqrt{17}}{2} \angle \tan^{-1}\left(-\frac{1}{4}\right) \text{ (white and pink)}$$

$$\overline{V} = 10\angle 0^\circ$$

$$\overline{I} = \frac{\overline{V}}{\overline{Z}_{eq}} = \frac{10\angle 0}{\sqrt{2}\angle -45} = 5\sqrt{2}\angle 45^\circ \text{ A (yellow)}$$

$$\overline{I} = \frac{\overline{V}}{\overline{Z}_{eq}} = \frac{10\angle 0}{\frac{\sqrt{17}}{2} \angle \tan^{-1}\left(-\frac{1}{4}\right)} = \frac{20}{\sqrt{17}} \angle -\tan^{-1}\left(-\frac{1}{4}\right) \text{ A (white and pink)}$$

c) (8 pts) Now replace the four capacitors with inductors $L_1=L_2=L_3=L_4=1 \mu\text{H}$ and calculate the equivalent impedance \overline{Z}_{AB} .

$$L_{eq} = (L_1 \parallel L_2) + (L_3 + L_4) = (.5) + (.5) = 1 \mu\text{H} \text{ (yellow)}$$

$$L_{eq} = (L_1 \parallel L_2) + (L_3 + L_4) = (1) + (1) = 2\mu\text{H} \text{ (white and pink)}$$

$$\overline{Z}_{AB} = j\omega L_{eq} = j(10^6 \text{ rads} / \text{s})(10^{-6} \text{ H}) = j\Omega \text{ (yellow)}$$

$$\overline{Z}_{AB} = j\omega L_{eq} = j(10^6 \text{ rads} / \text{s})(2 \times 10^{-6} \text{ H}) = 2j\Omega \text{ (white and pink)}$$

d) (6 pts) In this case, what is the current $i(t)$ in phasor form?

$$\overline{V} = 10\angle 0^\circ \text{ (all)}$$


$$\overline{Z}_{eq} = R + L_{eq} = 1 + j\Omega = \sqrt{2}\angle 45^\circ \text{ (yellow)}$$

$$\overline{I} = \frac{\overline{V}}{\overline{Z}_{eq}} = \frac{10\angle 0}{\sqrt{2}\angle 45} = 5\sqrt{2}\angle -45^\circ \text{ (yellow)}$$

$$\overline{Z}_{eq} = R + L_{eq} = 2 + 2j\Omega = 2\sqrt{2}\angle 45^\circ \text{ (white and pink)}$$

$$\overline{I} = \frac{\overline{V}}{\overline{Z}_{eq}} = \frac{10\angle 0}{2\sqrt{2}\angle 45} = \frac{5\sqrt{2}}{2}\angle -45^\circ \text{ (white and pink)}$$

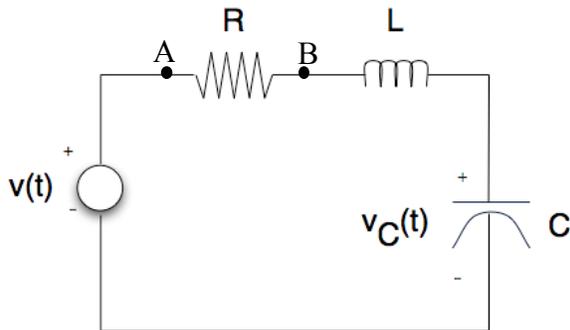3. (56 pts) We have a circuit with R, L, C and $v(t)$ as an input.



(a) (16 pts) If $v_C(t)$ is the voltage across the capacitor C , we can formulate the 2nd order circuit as follows.

$$\frac{d^2 v_C(t)}{dt^2} + A \frac{dv_C(t)}{dt} + B v_C(t) = f(t)$$

What are A, B, and $f(t)$? Express them in terms of R, L, C and $v(t)$.

$$A = \frac{R}{L}$$

$$B = \frac{1}{LC}$$

$$f(t) = \frac{v(t)}{LC}$$


(b) (5 pts) The undamped resonance frequency ω_0 is $\omega_0 = 10^4$ Hz and L is 10mH, what is the value of C ?

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(10^4 \text{ rad/s})^2 (0.01 \text{ H})} = 10^{-6} \text{ F}$$

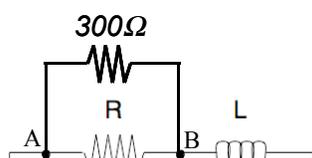(c) (10 pts) By adding another 300 Ohm resistor in parallel to the R , connecting at points A and B, see Figure below, we find the circuit is critically damped. What is the value of R ?

(NOTE: If you did not get the value for C from part b, full credit awarded for solution including C as a variable.)



$$\zeta = 1$$

Thus:

$$\alpha = \omega_o$$

$$\frac{R_{eq}}{2L} = 10^4 \text{ rad / s}$$


$$R_{eq} = 2L(10^4 \text{ rad / s}) = 2(.01H)(10^4 \text{ rad / s}) = 200\Omega$$

$$R_{eq} = \frac{R(300)}{R + 300} = 200\Omega$$

$$R = \frac{2}{3}(R + 300)$$

$$R = 600\Omega$$

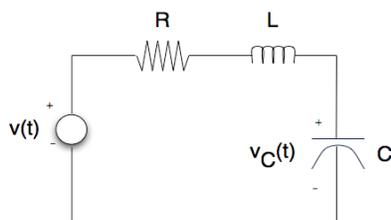(d) (5 pts) Is the original circuit (without the 300 Ohm parallel resistor, see Figure below) overdamped or underdamped?



$$\zeta = \frac{\alpha}{\omega_o}$$

Thus:

$$\alpha = \frac{R}{2L} = \frac{600}{2(.01H)} = 30000$$

$$\omega_o = 10^4 \text{ rad / s}$$

$$\zeta = 3$$

Thus the original circuit is overdamped.

Intuitively, the original circuit has a higher resistance, thus more energy is lost across the resistor, damping the circuit more than the critically damped case.


(e) (20 pts) We change the configuration of L and C to be in parallel as shown below, with the original values for R, L and C – the values you got from parts a- c.

What is the resonance frequency ω_0 ?

What is the damping ratio ζ ?

Is this circuit under-, critically, or over- damped?

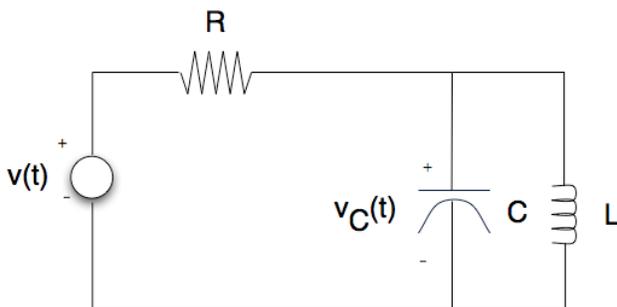(NOTE: If you did not get the values of RLC from parts a-c, you will get full credit if you can give all possible if-then's.)



If a Thevenin to Norton conversion is performed on the voltage source and resistor, it becomes apparent that this is a parallel RLC circuit. We then use the equations for a parallel RLC circuit:

$$\omega_o = \frac{1}{\sqrt{LC}} = 10^4 \text{ rad / s (same as in the series case)}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(600\Omega)(1\mu F)} = \frac{2500}{3}$$

$$\zeta = \frac{\alpha}{\omega_o} = \frac{2500}{3(10^4)} = \frac{1}{12}$$

$\zeta < 1$, so the circuit is underdamped.