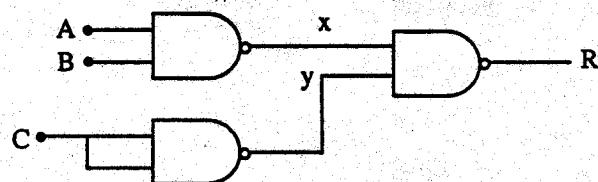



**Problem 1 (15 points)**

What is the value of the unknown node voltage in each of the following circuits? Assume diodes are perfect rectifiers.

(a)



(b)

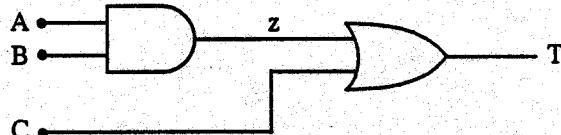


(c) Is  $R = T$  for all possible inputs?

YES  
 NO

(WARNING: You must fill out truth tables in this problem to receive credit.)


**Problem 2 (15 points)**

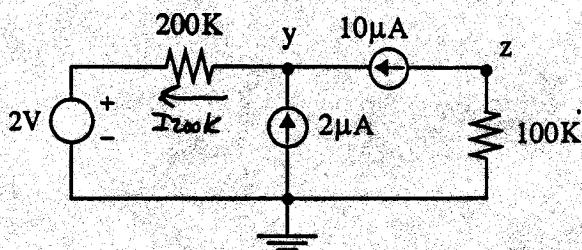

(a) Find  $V_y$ .  $V_y = 2V + I_{200k} \cdot 200k = 4.4V$

$\uparrow$   
 $12\mu A$

$V_y = 4.4V$

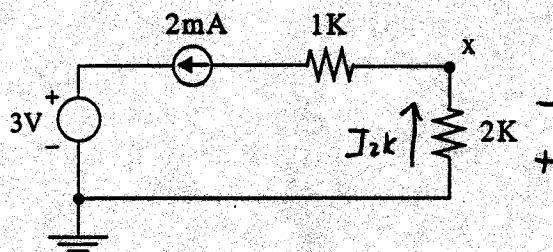


$I_{2k} = 2mA$

(b) Find  $V_x$ .

$V_x = -4V$

$V_x = 0 - 2k \cdot I_{2k} = -4V$

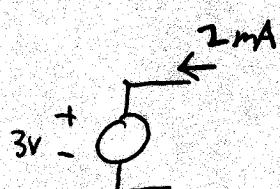(c) Find power delivered by the voltage source.



$P = V \cdot I$


$P = -2mA \cdot 3V = -6mW$

$P_3 = -6mW$

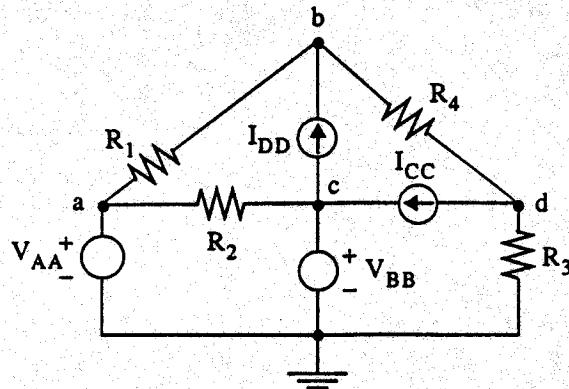**Problem 3 (12 points)**

For the circuit below:

- Identify known and unknown node voltages, and
- Write sufficient nodal equations to solve for the unknown node voltages (do not solve).



(a.1) known node voltages:

$$\underline{V_a = V_{AA}, V_c = V_{BB}}$$

(a.2) unknown node voltages:

$$\underline{V_b, V_d}$$

Nodal Equations:

at (b)


$$\underline{(V_{AA} - V_b)/R_1 + I_{DD} + (V_d - V_b)/R_4 = 0}$$

at (d)

$$\underline{(V_b - V_d)/R_4 - I_{CC} - V_d/R_3 = 0}$$

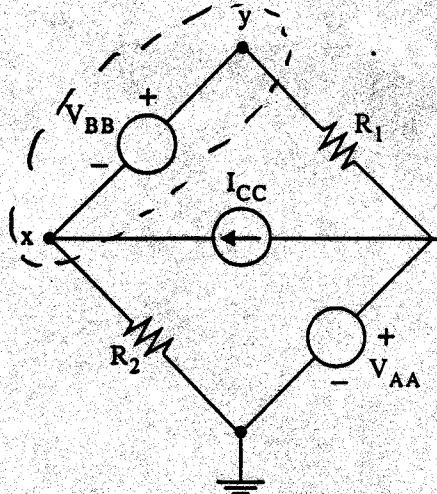Problem 4 (10 points)

For the circuit below, using nodal analysis write sufficient equations to find  $V_x$  and  $V_y$ . Do not solve.



Write KCL at the supernode

$$\frac{V_x}{R_2} + \frac{V_y - V_{AA}}{R_1} = I_{CC}$$


$$V_y - V_x = V_{BB}$$

Equations:

$$\frac{V_x}{R_2} + \frac{V_y - V_{AA}}{R_1} = I_{CC}$$

$$V_y - V_x = V_{BB}$$

Problem 5 (15 points)

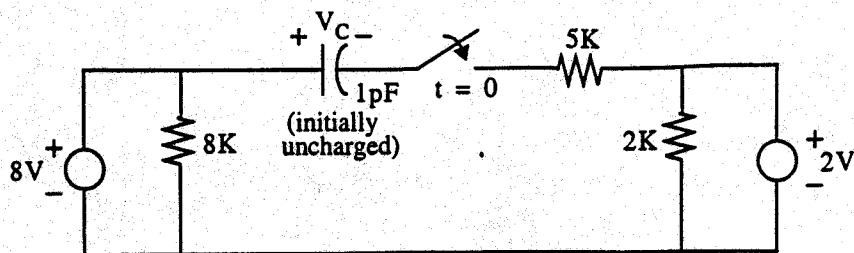

For the circuit above, the capacitor is initially uncharged. The switch closes at  $t = 0$ .

- (a) Find  $V_C$  for  $t = 0^+$  and  $t \rightarrow \infty$ .

Since initially the capacitor is uncharged,

$$V_C(0^+) = 0\text{ V}$$

at  $\infty$  the voltage at the (+) side


is  $8\text{ V}$ , at the (-) side of the

capacitor the voltage is  $2\text{ V}$ ,  $\Rightarrow V_C = 8 - 2 = 6\text{ V}$

$$V_C(t = 0^+) = 0\text{ V}$$

$$V_C(t \rightarrow \infty) = 6\text{ V}$$

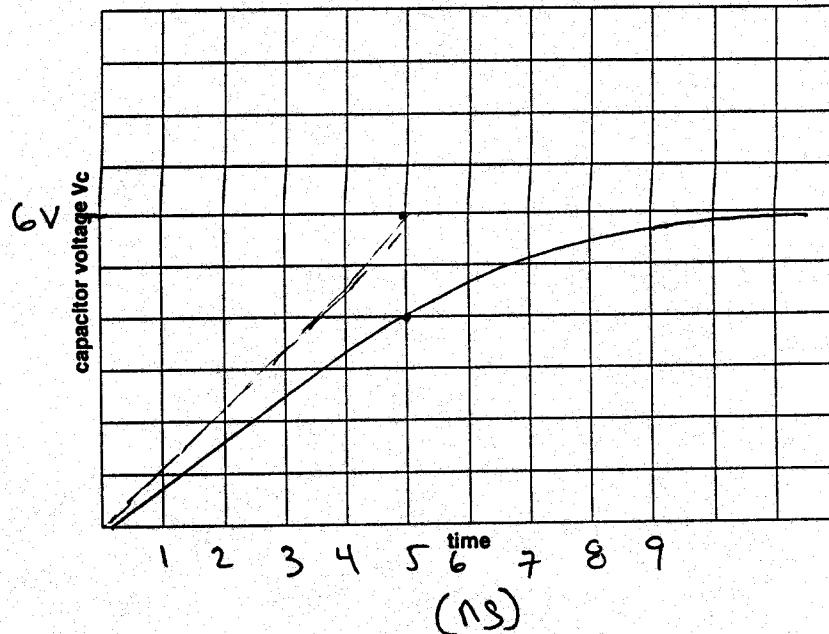- (b) Sketch (very neatly and accurately!)  $V_C$  vs.  $t$  on the graph below. You must label the axes.



$$\text{slope at } t=0 = \frac{6\text{ V}}{5\text{ ns}}$$

- (c) Write an equation for  $V_C(t)$ .

$$V_C(t) = 6 - 6e^{-t/\tau} \text{ V}$$

$$\text{For } \tau = R_{eq} C_{eq}$$


$$C_{eq} = 1\text{ pF}$$

$R_{eq} = 5\text{ k}\Omega$  since Voltage sources "short out" the  $8\text{ k}\Omega$  and the  $2\text{ k}\Omega$  resistors.

$$\tau = 5\text{ ns}$$
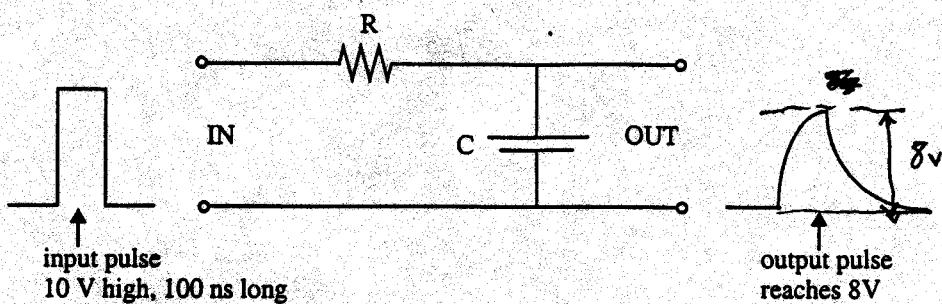
### Problem 6 (10 points)

In the lab on RC circuits, you measure the pulse response of the circuit below.



You know  $R$  is  $2\text{ k}\Omega$ . What is the value of  $C$ ?

For the rising portion of the output pulse

$$C = 31 \text{ pF}$$

$$V(t) = 10(1 - e^{-t/RC}).$$

$$\text{At } t = 100 \text{ ns}, V(100 \text{ ns}) = 8 \text{ V}. \quad R = 2 \text{ k}\Omega.$$

Therefore,



$$\frac{8}{10} = (1 - e^{-100 \times 10^{-9} / 2000 \text{ C}}).$$

Solving for  $C$ ,


$$C = \frac{10^{-10}}{2 \log 5} = 31.07 \text{ pF}$$

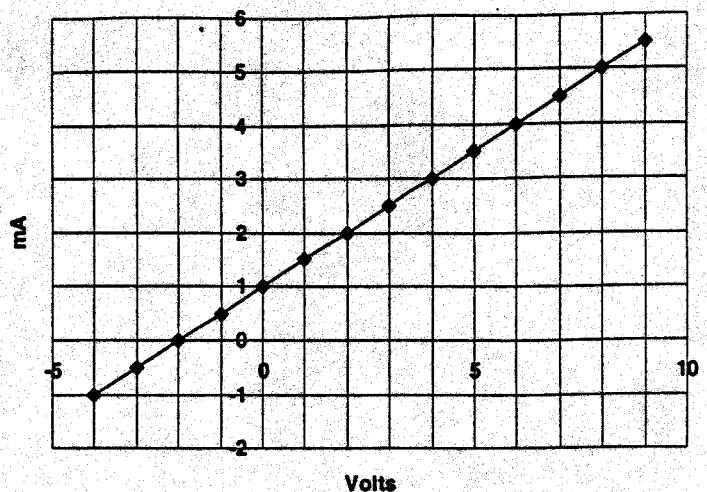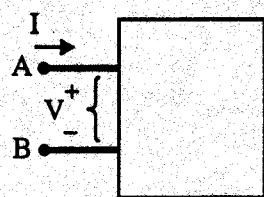**Problem 7 (11 points)**

You measure the I-V graph of a circuit in a “black box” in the lab.



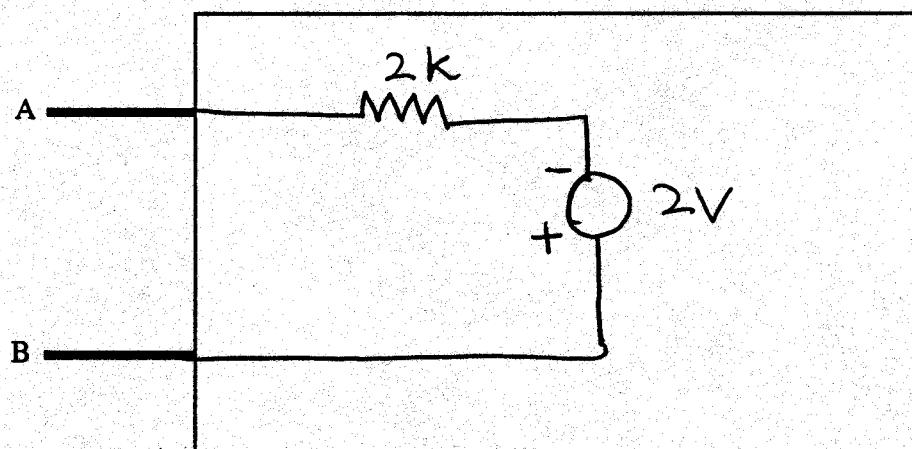What is a possible circuit that is in the box? Draw here ↓ .



Since the graph doesn't go through  $(0,0)$ , there's an active source inside the box.

$$\text{Slope} = \frac{I}{V} = \frac{1}{R} = \frac{2 \times 10^{-3}}{4}$$

$$\Rightarrow R = 2 \text{ k}\Omega$$

Let's assume there is a voltage source in series with  $R$ . Let this be  $V_s$  when  $I = 0$ .

when  $I = 0$ ,  $V = -2$  volts


$$V = IR + V_s \Rightarrow -2 = 0 + V_s$$

$$\Rightarrow V_s = -2 \text{ Volts.}$$


Thus, a possible circuit is as the one given in fig-a.
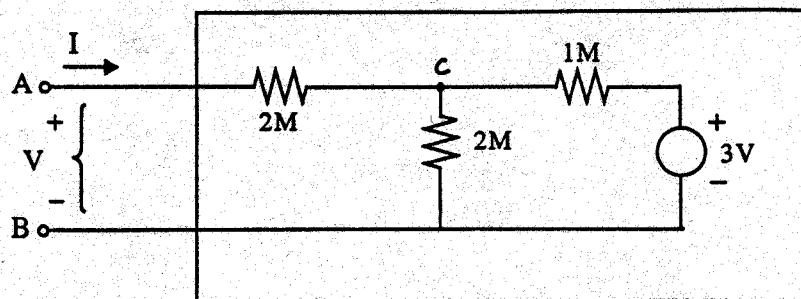
### Problem 8 (12 points)

In this experiment you “peek,” i.e., you open the box before testing it. You see the following circuit:



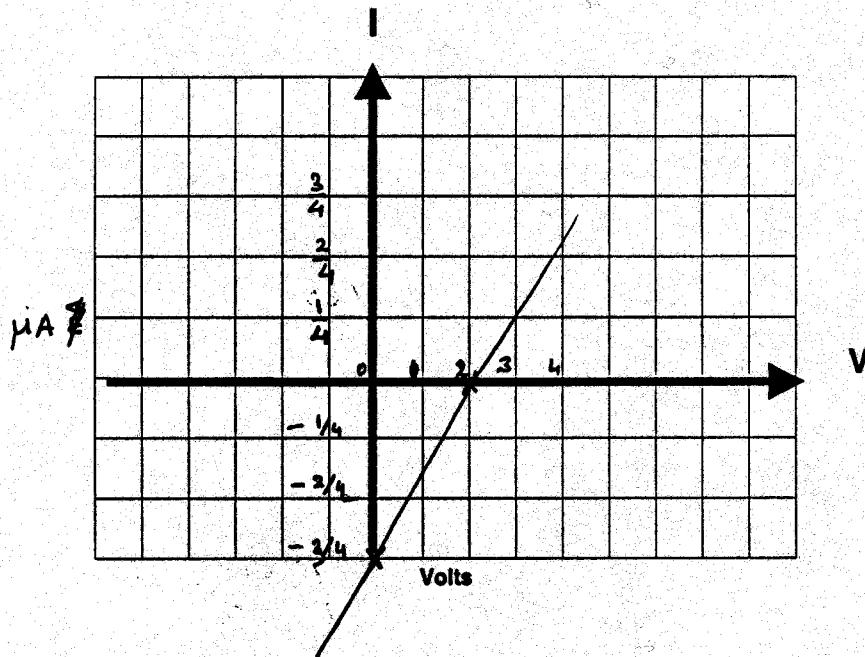What will be the I-V graph you will measure for this circuit? (You must label axes for credit.)



The easiest way to draw the I-V curve  
is to find  $V_{oc}$  and  $I_{sc}$

$V_{oc}$  (Open Circuit Voltage)

Since  $I = 0$ ,  $V_A = V_C$ .


$$V_C = \left( \frac{2M}{2M+1M} \right) 3V = 2 \text{ Volts.}$$

$$= V_{oc}.$$

$I_{sc}$  (Short Circuit Current)

Since  $V_A = 0$  (ie  $V_A = V_B$ )

equivalent circuit can be drawn as

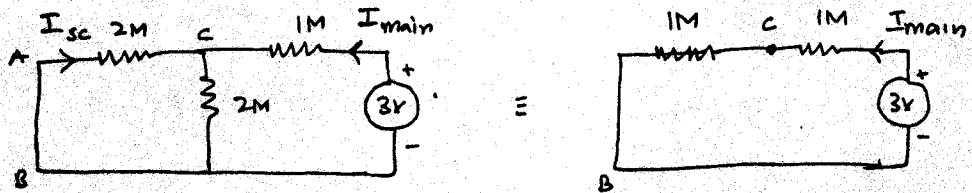

$$I_{main} = \frac{3V}{2M} = 1.5 \mu A.$$

$$\text{Therefore } I_{sc} = -\frac{1}{2} I_{main} = -\frac{3}{4} \mu A$$

so we get  $V_{oc} = 2 \text{ Volts}$ ,  $I_{sc} = -0.75 \times 10^{-6} \text{ A}$

This gives us the required I-V graph !!