
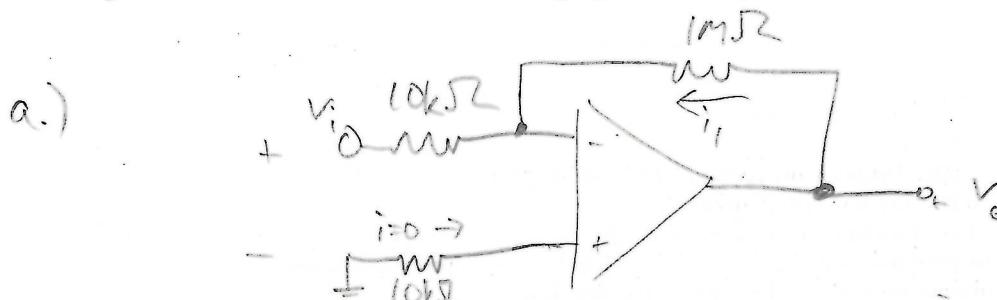


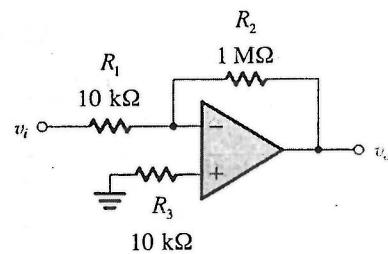1. Consider the Op Amp circuit on the right.
- Derive the voltage gain expression of the amplifier if we consider the Op Amp to be ideal (infinite open-loop gain, infinite input resistance, zero output resistance)?
  - What is the input resistance of the amplifier?
  - What is the value of the voltage gain for a signal with  $10\text{ k}\Omega$  source resistance?



$$V_+ = 0 \Rightarrow V_- = 0$$

$$i_i = \frac{V_o - 0}{1M\Omega} = \frac{-(V_i - 0)}{10k\Omega}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{1M\Omega}{10k\Omega} = -100 (\text{v/v})$$

$$\boxed{\frac{V_o}{V_i} = -100 (\text{v/v})}$$


final numbers  
account for 2  
points each  
sub question

⑧

b.)  $i_i = \frac{V_i}{10k} \Rightarrow R_{in} = \frac{V_i}{i_i} = 10k\Omega$

$$\boxed{R_{in} = 10k\Omega}$$

⑥

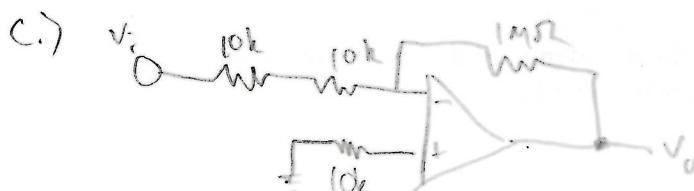


$$\frac{V_o}{V_i} = A_v \left( \frac{R_{in}}{R_{in} + R_s} \right) = -100 \cdot 5 = -50$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = -50 (\text{v/v})}$$

⑥

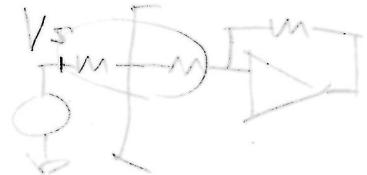2. For the same circuit as in Problem 1 and the same source resistance, but consider an Op Amp with a finite open loop gain of  $A_0 = 100,000$ , and an open-loop bandwidth of 100 Hz. The input resistance of the Op Amp is still infinite, and the output resistance is zero.
- (10) a. What is the 3-dB frequency of the amplifier in unit of Hz?  
*(You don't need to re-derive the expression if you can deduce the frequency response of the close-loop amplifier).*
- (10) b. Show the frequency response in Bode plot. Mark the 3-dB frequency, unity gain frequency, the low frequency gain in dB, and the slope in dB/decade.



a.) Fixed gain-bandwidth product

$$|A| \cdot f_{3dB} = 10^5 \cdot 10^2 \text{ Hz} = 10^7 \text{ Hz}$$

Amplifier in Prob. 1  $|A| = 50$


-5 if  
Source neglect  
resistance

$$\Rightarrow f_{3dB} = \frac{10^7}{|A|} = \frac{10^7}{50} = 2 \cdot 10^5 = 200 \text{ kHz}$$

$$f_{3dB} = 200 \text{ kHz}$$

$$\begin{aligned} \frac{10^7}{100} \\ = 10^5 \text{ Hz} \\ = 100 \text{ kHz} \end{aligned}$$


b.)

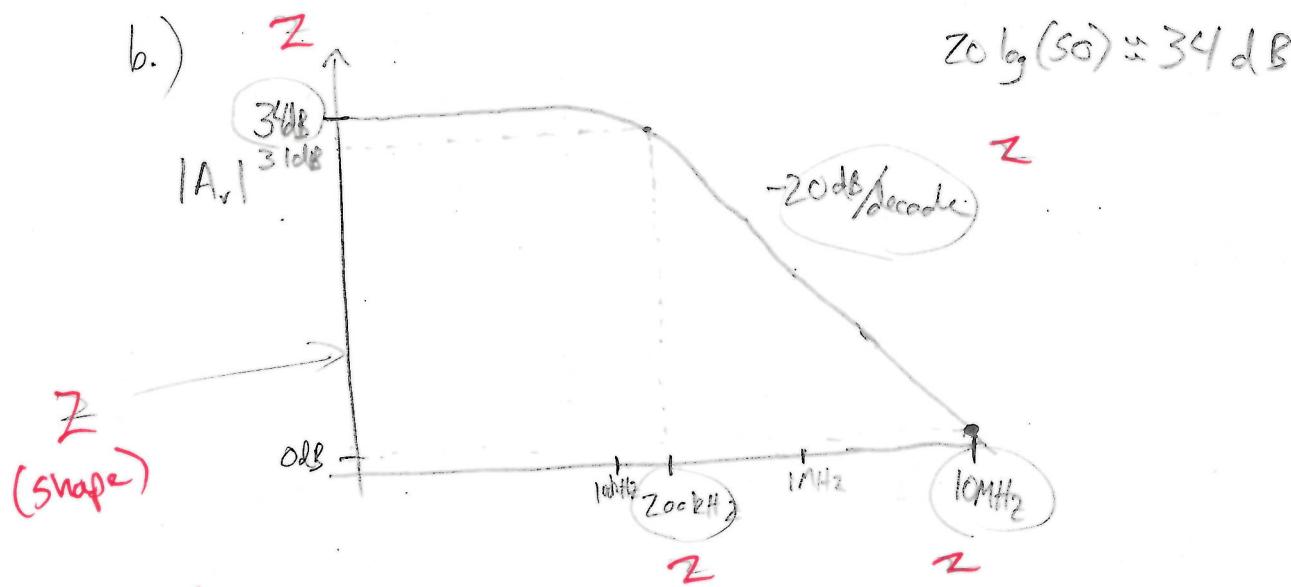

Half points deducted for crossover from part a)

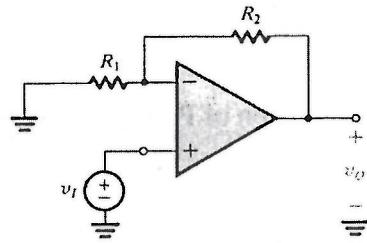3. A non-inverting amplifier with variable gain is shown on the right. Here,  $R_1 = 1 \text{ k}\Omega$  and  $R_2$  is variable from  $100 \text{ k}\Omega$  to  $100 \text{ M}\Omega$ . This input signal is:
- $$v_i(t) = (10 \text{ mV}) \cdot \sin(2\pi \cdot 10 \text{ kHz} \cdot t)$$

The Op Amp has a slew rate (SR) of  $6.28 \text{ V}/\mu\text{s}$ .



- First, assume the Op Amp has infinite bandwidth. If we gradually increase the gain of the amplifier by increasing  $R_2$ , at what value of  $R_2$  does the output become slew rate limited?
- Now consider the Op Amp with a finite gain-bandwidth product of  $100 \text{ MHz}$  and  $R_2 = 20 \text{ M}\Omega$ , is the amplifier bandwidth-limited or SR-limited? Show the calculation supporting your answer.

a. Gain  $\underline{Av = 1 + \frac{R_2}{R_1}}$  account for 3f

$$V_o = Av \cdot v_i$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = Av \cdot 10 \text{ mV} \cdot 2\pi \cdot 10 \text{ k} \cdot \cos(2\pi \cdot 10 \text{ kHz} \cdot t) \quad |_{2\pi \cdot 10 \text{ kHz} \cdot t = 0} \\ \underline{\underline{= Av \cdot 10 \text{ mV} \cdot 2\pi \cdot 10 \text{ k}}} \leq SR = 6.28 \text{ V}/\mu\text{s} \quad 4 \\ = 2\pi \cdot 10 \text{ kHz} \cdot \frac{10^2}{10^3} \text{ final number } 2$$

$$Av \leq \frac{10^2}{0.01} = 10^4 \Rightarrow R_2 \leq 10 \text{ M}\Omega \quad (10)$$

b. Given  $R_2 = 20 \text{ M}\Omega$ ,  $Av_o = 1 + \frac{20 \text{ M}}{10 \text{ k}} \approx 2 \times 10^4$

$$f_{3\text{dB}} = \frac{100 \text{ kHz}}{2 \times 10^4} = \boxed{5 \text{ kHz}} < 10 \text{ kHz} \quad \text{account for 3 points}$$

At first, the Op Amp is BW limited (5)

then, consider the BW caused attenuation

if answer SR limited (with math)  $Av_{@10 \text{ kHz}} = \frac{Av_o}{\sqrt{1 + (\frac{f}{f_{3\text{dB}}})^2}} \quad f = 10 \text{ kHz} = \frac{2 \times 10^4}{\sqrt{5}}$

but forget BW attenuation penalty (-2) So  $\left. \frac{dV_o}{dt} \right|_{\max} = \frac{2 \times 10^4}{\sqrt{5}} \times 10 \text{ mV} \cdot 2\pi \cdot 10 \text{ k} < SR$

| NO SR limited (5)

4. A pn junction in the reverse-bias configuration can be used as a variable capacitor. In the lab, we measured the capacitances of a pn junction diode at two voltages:
- At 2.4 V reverse bias, the capacitance is measured to be 0.5 pF
  - At 12 V reverse bias, the capacitance is measured to be 0.25 pF
- 10 a. Find the capacitance of the pn junction diode at zero bias.  
10 b. Find the built-in potential of the pn junction diode.

Given:  $C_{j0} = A \sqrt{\left(\frac{q}{2}\right) \frac{N_A N_D}{N_A + N_D}} \cdot \frac{1}{\sqrt{V_0}}$

$$= \frac{\alpha}{2\sqrt{V_0}}$$

We know with reverse bias  $V_0 \Rightarrow V_0 + V_R$

$$\Rightarrow C_j = \frac{\alpha}{2\sqrt{V_0 + V_R}}$$

$$\Rightarrow C_j = C_{j0} \cdot \frac{\sqrt{V_0}}{\sqrt{V_0 + V_R}} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}}$$

$$C_j^2 \left(1 + \frac{V_R}{V_0}\right) = C_{j0}^2$$

(a)  $V_R = 2.4 \text{ V}$ ,  $C_j = 0.5 \text{ pF}$

$$\Rightarrow .25 \left(1 + \frac{2.4}{V_0}\right) = C_{j0}^2$$

(b)  $V_R = 12 \text{ V}$ ,  $C_j = 0.25 \text{ pF}$

$$\Rightarrow .0625 \left(1 + \frac{12}{V_0}\right) = C_{j0}^2 = .25 \left(1 + \frac{2.4}{V_0}\right)$$

$$1 + \frac{12}{V_0} = 4 + \frac{9.6}{V_0} \Rightarrow V_0 + 12 = 4V_0 + 9.6$$

$$\Rightarrow 3V_0 = 2.4, \boxed{V_0 = 0.8 \text{ V}}$$

-2 if close  
w/ correct approach  
-5 if correct approach but not close

$$C_{j0}^2 = .25 \left(1 + \frac{2.4}{0.8}\right) = 1 \Rightarrow \boxed{C_{j0} = 1 \text{ pF}}$$

Page | 7

10

5. Consider the following two one-sided pn junction diodes with opposite doping profiles:

Diode A:  $N_D = 10^{18} \text{ cm}^{-3}$ ,  $N_A = 10^{16} \text{ cm}^{-3}$   
 Diode B:  $N_D = 10^{16} \text{ cm}^{-3}$ ,  $N_A = 10^{18} \text{ cm}^{-3}$

The rest of the material parameters are shown in the table. Other parameters (e.g., junction area) of the two diodes are identical.

- What is the ratio of the current going through the diodes under a forward bias voltage of 0.8V?
- What is the difference of the built-in voltages between these two diodes?
- What is the ratio of the diode capacitances at zero bias?

Electron diffusion coefficient	$D_n$	$30 \text{ cm}^2/\text{s}$
Hole diffusion coefficient	$D_p$	$10 \text{ cm}^2/\text{s}$
Electron diffusion length	$L_n$	$2 \mu\text{m}$
Hole diffusion length	$L_p$	$1 \mu\text{m}$

a)

$$\text{Diode current eqn: } I = Aq n_i^2 \left( \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right) (e^{V_{FT}} - 1)$$

$$\text{Diode A: } I_A = Aq n_i^2 \frac{D_p}{L_p N_A} (e^{V_{FT}} - 1)$$

$$\text{Diode B: } I_B = Aq n_i^2 \frac{D_n}{L_n N_D} (e^{V_{FT}} - 1)$$

$$\Rightarrow \frac{I_A}{I_B} = \frac{D_p}{D_n} \cdot \frac{L_p}{L_n} \cdot \frac{N_D}{N_A} = \frac{10}{30} \cdot \frac{1}{2} \cdot \frac{10^{16}}{10^{16}} = \boxed{\frac{1}{3}}$$

~~incorrect~~ wrong number  
take 2 points off

b.)

$$V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right) \quad N_A N_D = 10^{16} \cdot 10^{16} = 10^{34} \text{ for both diodes}$$

$$\Rightarrow V_{0A} = V_{0B} \Rightarrow V_{0A} - V_{0B} = \boxed{0V}$$

c.)

$$C_{j0} = A \sqrt{\frac{e \pi}{2}} \frac{N_A N_D}{N_A + N_D} \cdot \frac{1}{\sqrt{V_0}} \quad \frac{N_A N_D}{N_A + N_D} \text{ is the same for both A and B}$$

$$V_{0A} = V_{0B}$$

$$\Rightarrow C_{j0A} = C_{j0B}$$

$$\Rightarrow \frac{C_{j0A}}{C_{j0B}} = \boxed{1}$$