

UNIVERSITY OF CALIFORNIA, BERKELEY  
Department of Electrical Engineering and Computer Sciences

EE 100  
Intro. To Electronics Engineering

Spring 2005  
Bharath "Bart Simpson" Muthuswamy

Final Exam  
May 13<sup>th</sup> 2005  
Time Allotted: 3 hours

NAME: \_\_\_\_\_  
(print) Last First

SOLUTIONS / GRADING SCHEME

STUDENT ID#: \_\_\_\_\_

I WILL NOT CHEAT ON THIS EXAM. Signature: \_\_\_\_\_

Note(s):

1. You will receive [3 pts] for filling out the information above.
2. MAKE SURE THE EXAM HAS 10 NUMBERED PAGES.
3. This is a CLOSED BOOK exam. However, you may use THREE 8.5 x 11" of notes (both sides) and a calculator.
4. SHOW YOUR WORK on this exam. MAKE YOUR METHODS CLEAR TO THE GRADER so you can receive partial credit.
5. WRITE ANSWERS CLEARLY IN THE SPACES (lines or boxes) PROVIDED.
6. Remember to specify units on answers whenever appropriate.
7. PLEASE NOTE: THE NUMERICAL ANSWER TO THE PROBLEMS MAY NOT BE WHOLE NUMBERS (i.e., THEY COULD BE NEGATIVE or DECIMAL).

SCORE: This page: 3 / 3

1: \_\_\_\_\_ / 22

2: \_\_\_\_\_ / 25

3: \_\_\_\_\_ / 25

4: \_\_\_\_\_ / 25


TOTAL: \_\_\_\_\_ / 100

Problem 1 (22 points)

In the circuit below:

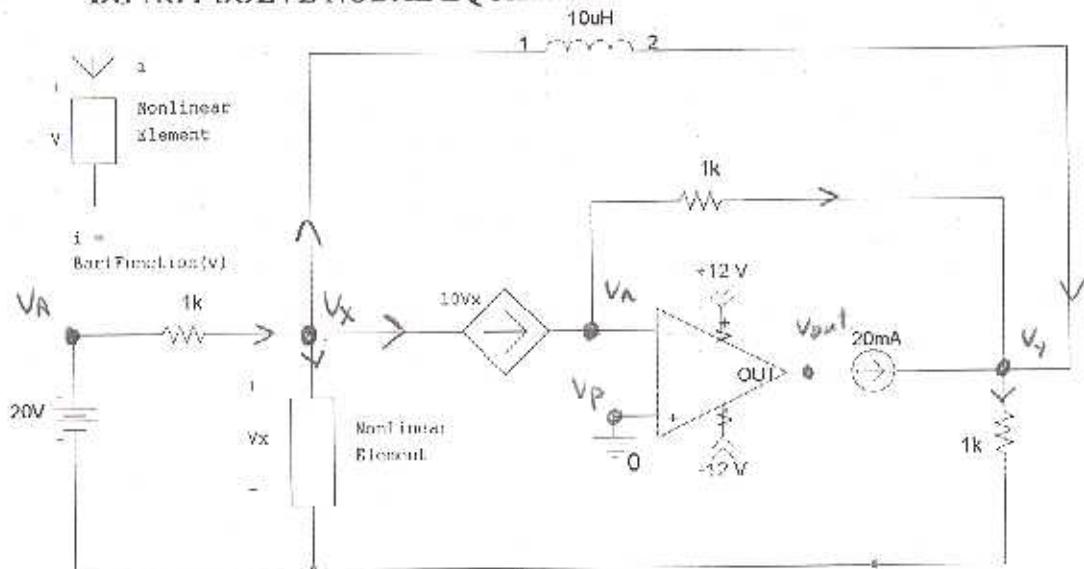**NOTE: DO NOT ASSUME  $V_p = V_n$  for the op-amp.**

- Mark the known node voltage(s) with CORRECT voltage values.
- Label the unknown node voltages.
- Write sufficient nodal equations to solve for the unknown node voltages in (b). **DO NOT SOLVE NODAL EQUATIONS.**



node's:

$V_A, V_x, V_p, V_n, V_{out}$

Missing a voltage for a or b  $\rightarrow -1$

Sign Error in an equation  $\rightarrow -3$  per error

Missing an equation  $\rightarrow -5$

Equation just wrong (period)  $\rightarrow -4$

Integrated for  $i_L$  (assume  $V = \text{const}$ )  $\rightarrow -2$

(a) Known node voltages:  $V_A = 20V, V_p = 0V$  +2

(b) Unknown node voltages:  $V_x, V_y, V_n, V_{out}$  +4

(c) Write final nodal equations in the box. Make sure equations are SUFFICIENT.

$$\begin{aligned} \bullet V_x: \frac{20-V_x}{1k} &= \text{Barf function}(V_x) + 10V_x + i_L \\ V_x - V_y &= L \frac{di_L}{dt} \end{aligned}$$

$$\text{or } \frac{20-V_x}{1k} = \text{Barf function}(V_x) + 10V_x + \frac{1}{L} \int_0^t (V_x - V_y) dt$$

$$\bullet V_y: \frac{V_n - V_y}{1k} + 20\text{mA} + i_L = \frac{V_y}{1k} \Rightarrow \frac{V_n - V_y}{1k} + 20\text{mA} + \frac{1}{L} \int_0^t (V_x - V_y) dt = \frac{V_y}{1k}$$


$$\bullet V_n: 10V_x = \frac{V_n - V_y}{1k}$$

$$\bullet V_{out}: V_{out} = A(V_p - V_n) = A(0 - V_n) = -AV_n$$

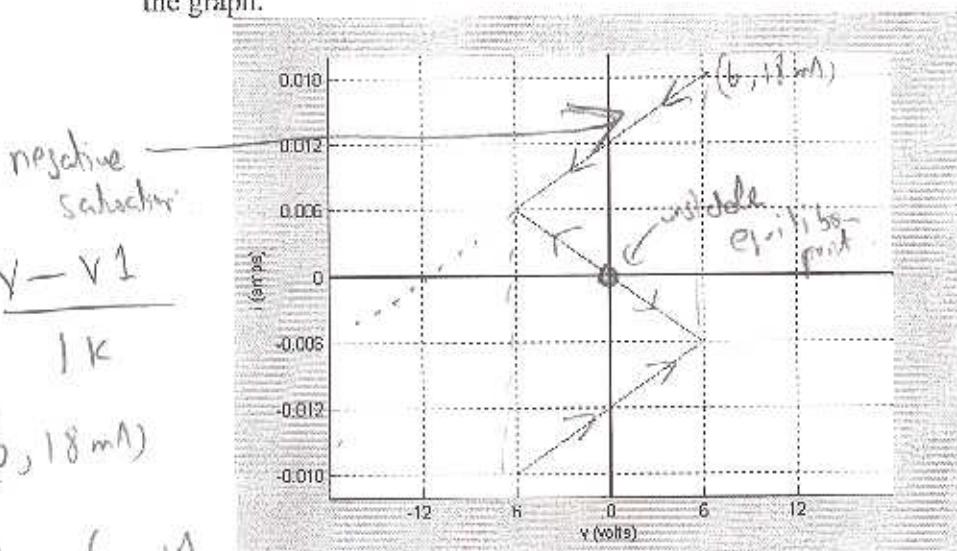Problem 2 (25 points)

In the circuit below, assume  $(v(0), i(0))$  is  $(6 \text{ V}, 18 \text{ mA})$ . Assume  $C_2$  is initially discharged. DO NOT IGNORE THE EFFECTS OF THE RAIL VOLTAGES FOR THE OP-AMPS. You may use  $\ln(1/3) = -1.1$

- 1 (a) On the driving point characteristic for the nonlinear op-amp, label the equilibrium point(s), stability of the equilibrium point(s) and dynamic route. 2 (5)
- (b) Sketch  $v_1(t)$  (output voltage of first op-amp) for  $t \geq 0$  and for one time period. Clearly mark the periods, maximum voltage value and minimum voltage value on the graph. 4 (10)
- (c) Sketch  $v_2(t)$  (output voltage of second op-amp) for  $t \geq 0$  and for one time period. Clearly mark the periods, maximum voltage value and minimum voltage value on the graph. 4 (10)



$$i = -C \frac{dv}{dt}$$

$$i > 0, v' < 0$$

$$i < 0, v' > 0$$

$$I = \frac{V - V_1}{1k}$$

$$\text{at } (6, 18 \text{ mA})$$

$$18 \text{ mA} = \frac{6 - V_1}{1k} \Rightarrow V_1 = 6 - 18 \text{ mA}$$

$$V_2 = 6 - V_1$$

$$V_2 = -12 \text{ V}$$


plan : ?

$$v(t) = v_f + (v_i - v_f)e^{-t/T_C}$$


$$\Rightarrow v(0) = -12 + (6 + 12)e^{-0/1\text{sec}}$$

$$\Rightarrow v(0) = -12 + 18e^{-t/1\text{sec}} \quad \therefore v(t_1) = -6$$
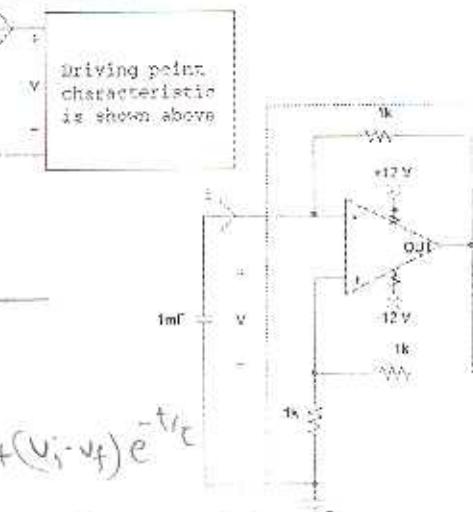
$$\Rightarrow -\frac{t_1}{1\text{sec}} = \ln\left(\frac{1}{3}\right) \Rightarrow t_1 = 1.1 \text{ sec}$$



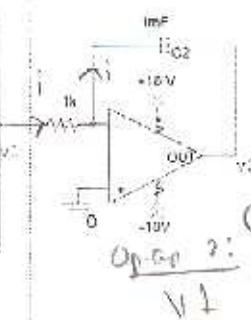Driving point characteristic is shown above



Assume  $dC/dV = 0$

$$\frac{V_1}{1k} = C \frac{d}{dt} (0 - V_2)$$

$$\Rightarrow V_2 = - \int V_1 dt$$

# Algebraic Integration ( $V_2$ determined)



$$V_2 = \int_0^t 12 dt + V_{\text{initial}} \rightarrow V ((2 \text{ initially}) \text{ discharge})$$

$$= 12 \cdot t \Big|_0^1 = 12 \cdot 1 = 12 \text{ V} \quad (< 18 \text{ V} \Rightarrow \text{op-amp } 2 \text{ does not run})$$

$$V_2 = - \int_{-1}^{2.2} (12) dt + 12 \cdot 2 \text{ V} \quad \begin{array}{l} \text{don't forget} \\ V_{\text{initial}} \text{ from} \\ \text{eqn } (1) \end{array}$$


$$= - 12(1.1) + 12 \cdot 2 \text{ V} = 0 \text{ V}$$

visually  
integrate

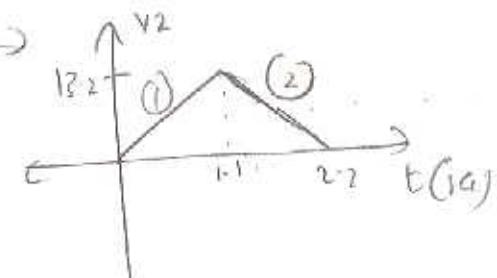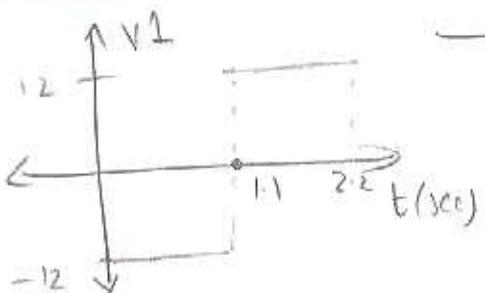


- Work → ~~-15 to -25~~ (2)  $V_p = V_n = 0 \rightarrow -15$  points  
 4/100% (3) op-amp is not rail-to/rail/wrong rail → -15  
 Problem 3 (25 points) (4) wrong diode D2 voltage → -15 points

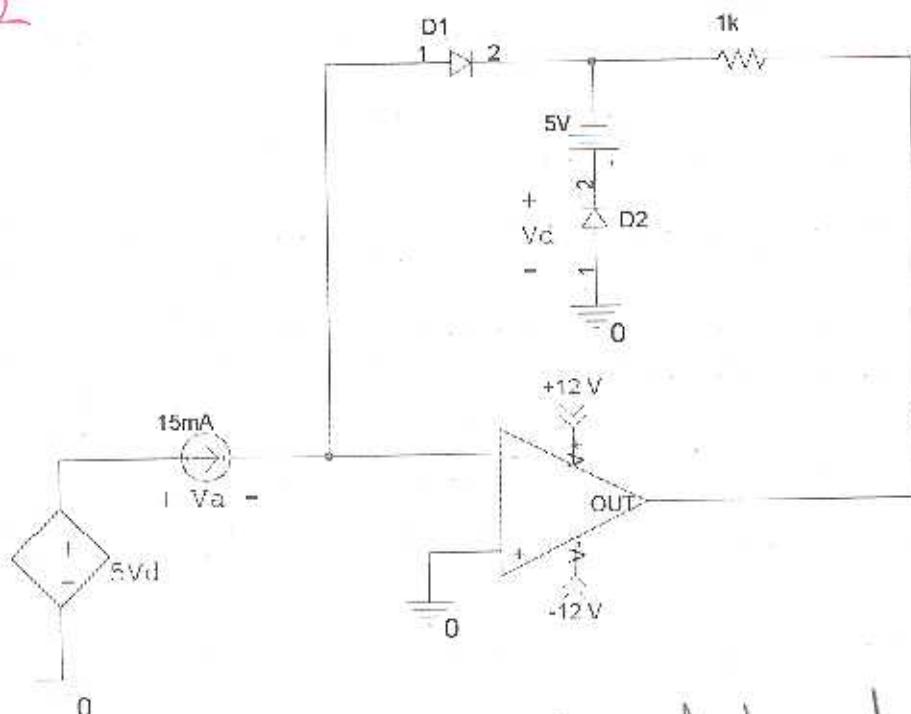In the circuit below, find  $V_a$ . **DO NOT IGNORE THE EFFECTS OF THE OP-AMP RAIL VOLTAGES.** Assume all diodes are ideal.



First to start with diodes: Look at circuit, diode

1 places on Q D2 seems off:

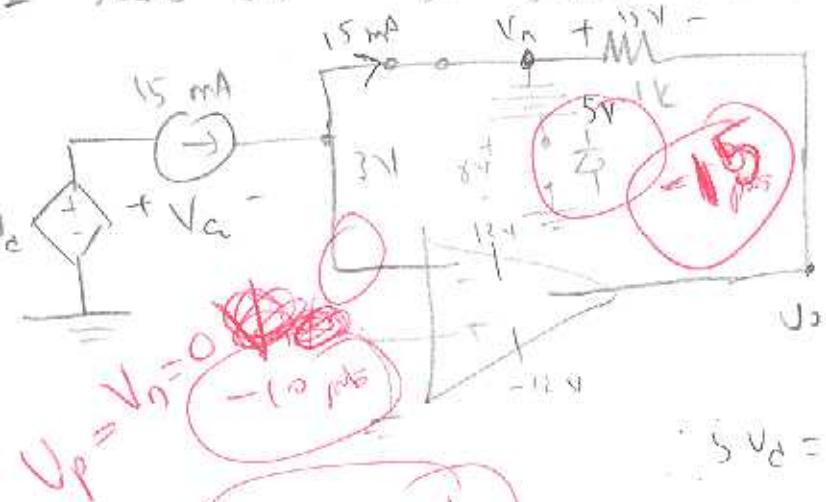

$$\text{If } V_h = V_p = 0, \Rightarrow V_2 = -15$$

→ Obviously, op-amp rail

$$\Rightarrow V_o = -12 \text{ V}$$

$$V_h = -12 \text{ V} + 15 \text{ V} = 3 \text{ V}$$

(Check:  $V_D = 8 \text{ V} \Rightarrow D2$  is)

$$5V_d = 42 \text{ V}$$

$$V_a = \underline{\quad 37 \text{ V} \quad}$$

Op-amp is not rail-to/rail/wrong rail  
 -15

$$V_a = 42 - 3 = 37 \text{ V}$$


Wrong diode state, -15 ps

Hey Justin, do this

problem ☺

Problem 4 (25 points)

-10 wrong  
graphing addition

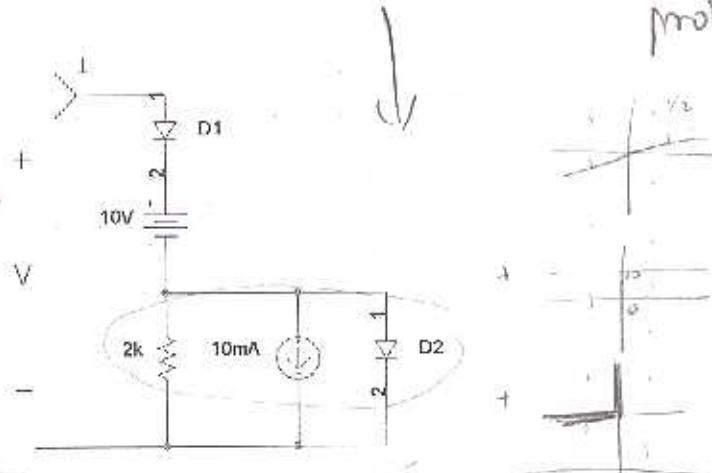

Using the grid shown below, plot the I-V graph of the circuit above. Assume all diodes are ideal.

