

Name: _____

SID: _____

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering and Computer Sciences

B. CAGDASER

Final
May 20, 2005

EECS 240
SPRING 2005

Show derivations and mark results with box around them. Erase or cross-out erroneous attempts. Simplify algebraic results as much as possible! Mark your name and SID at the top of the exam and all extra sheets.

You may need the following integrals:


$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o}} \right|^2 df = \frac{\omega_o}{4}$$

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4}$$

$$\int_0^{\infty} \left| \frac{\frac{s}{\omega_o}}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4}$$

	Total pts	Score
Q1	20	
Q2	20	
Q3	30	
Q4	20	
Q5	10	
Total	100	

Question 1 (20pts)

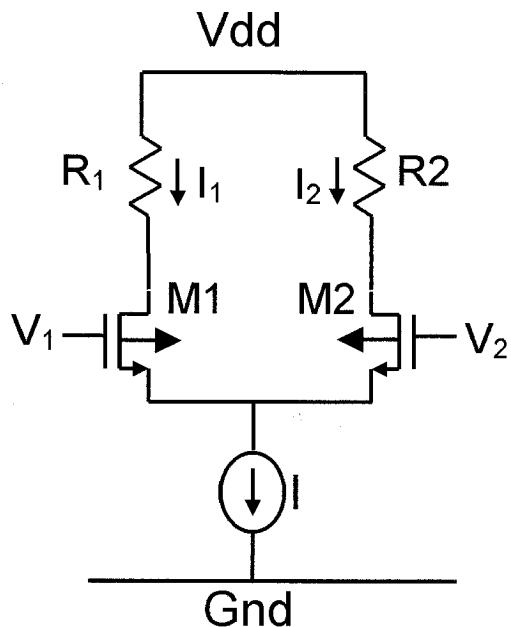

In the fully-differential amplifier above:

- (10pts) Calculate the input referred offset voltage for $\Delta V_{TH}=2\text{mV}$, $\Delta(W/L)/(W/L)=1\%$, $\Delta R/R=1\%$. M1 and M2 have $V^*=200\text{mV}$.
- (10pts) Assume only the following mismatches exist (different than the part a): $\Delta R/R=1\%$, $\Delta g_{mb}/g_{mb}=1\%$. Calculate the CMRR. $g_{mb} = 0.1 g_m$

$$a) \Delta V_o = \Delta I \cdot R + \Delta R \cdot I$$

$$\Delta I = I \cdot \frac{\Delta w/L}{w/L} + g_m \cdot \Delta V_{TH}$$

$$\Delta V_{in} = \frac{\Delta V_o}{g_m R} \quad \frac{V_o}{V_{in}} = g_m \cdot R$$

$$\Delta V_{in} = \frac{R}{g_m R} \left[I \cdot \frac{\Delta w/L}{w/L} + g_m \cdot \Delta V_{TH} \right] + \frac{\Delta R \cdot I}{g_m \cdot R}$$

$$\Delta V_{in} = \frac{I}{g_m} \cdot \frac{\Delta w/L}{w/L} + \Delta V_{TH} + \frac{I}{g_m} \cdot \frac{\Delta R}{R}$$

$$\frac{I}{g_m} = \frac{V^*}{2} \Rightarrow \Delta V_{in} = 100\text{mV} \cdot 0.01 + 2\text{mV} + 100\text{mV} \cdot 0.01$$

$$\Delta V_{in} = 4\text{mV} //$$

$$b) \frac{V_{od}}{V_{cm}} = \Delta gmb \cdot R \cdot V_{cm} + \Delta R \cdot gmb \cdot V_{cm}$$

we ignore $\Delta R \cdot \frac{gm}{gmb(R+1)}$
 $\frac{gm}{gmb(R+1)}$ is small

$$\text{Ad-cm} = \Delta gmb \cdot R + \Delta R \cdot gmb = \frac{V_{od}}{V_{cm}}$$


$$\text{Ad} = \frac{V_{od}}{V_{id}} = gm \cdot R$$

$$CMRR = \frac{\text{Ad}}{\text{Ad-cm}} = \frac{gm \cdot R}{\Delta gmb \cdot R + \Delta R \cdot gmb} = \frac{1}{\frac{\Delta gmb}{gm} + \frac{\Delta R}{R} \cdot \frac{gm}{gm}}$$

$$gmb = 0.1 \text{ gm} \Rightarrow \Delta gmb = 0.001 \text{ gm}$$


$$CMRR = \frac{1}{0.001 + 0.001} = 500 = 54 \text{ dB}_{//}$$

Question 2 (20pts)

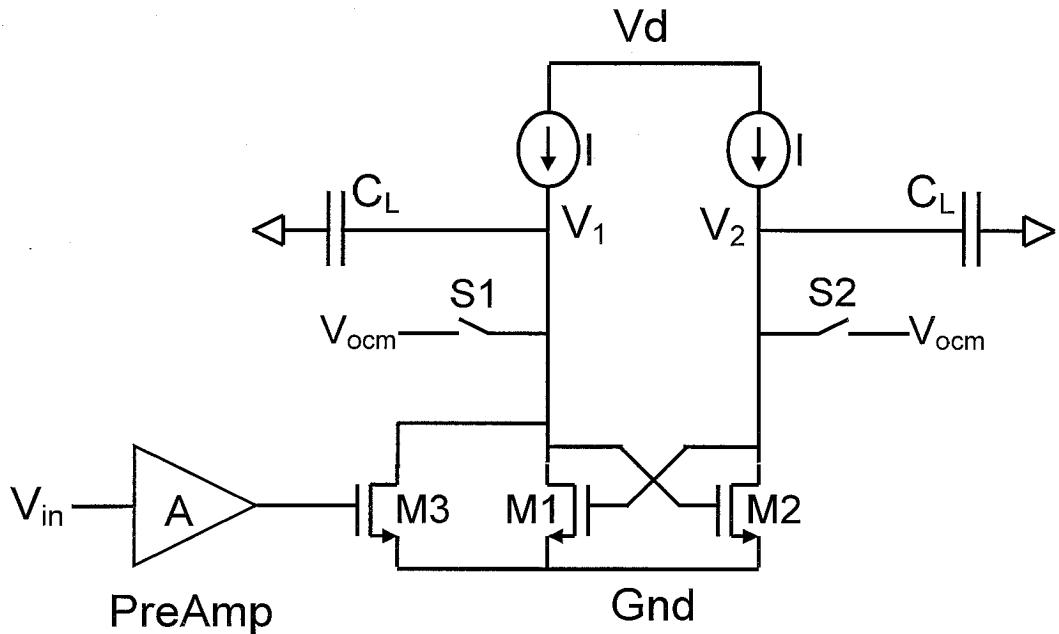

In the comparator circuit shown above, V_1 and V_2 are initialized to V_{ocm} . Due to the implementation errors switch S_2 introduces an offset voltage of V_{os} . Given the offset voltage V_{os} , what is the minimum V_{in} that this comparator can successfully detect?

Small signal model:

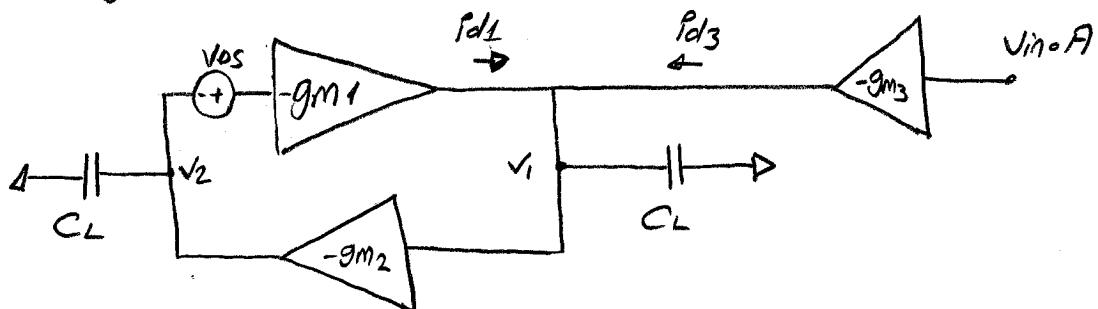


- V_2 & V_1 are initialized to 0 : small-signal
- For $V_{os} < 0$, P_{d1} cancels P_{d3} . P_{d1} must be smaller than P_{d3} for the correct transition.

$$P_{d1} < P_{d3}$$

$$V_{os} \cdot g_{m1} < g_{m3} \cdot A \cdot V_{in}$$

$V_{os} \cdot \frac{g_{m1}}{g_{m3} \cdot A} < V_{in} \Rightarrow$ Pre-amp decreases the influence of the V_{os} .

Question 3 (20pts)

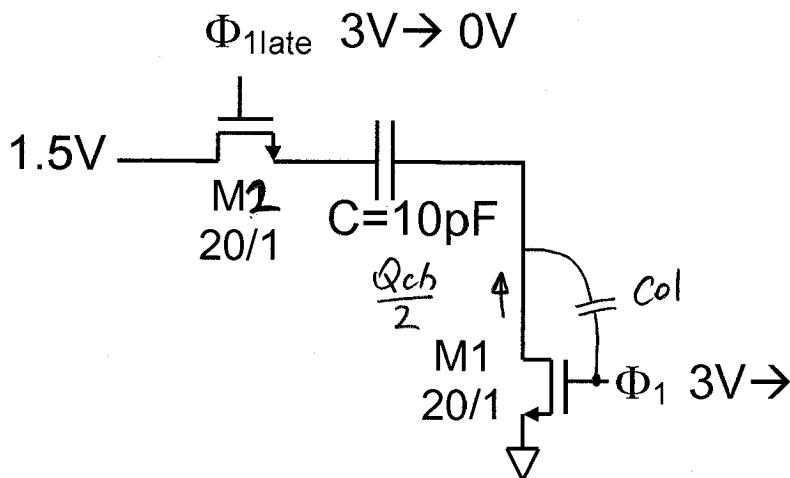

In the sampling circuit above, find the total sampling error for a sampling time of $t_s = 2.5\text{ns}$. Assume fast gating and 50% charge split. Hint: $e^{-4} \sim 0.02$.

Parameter:

$$V_{THN}=1V, \mu_n C_{ox}=200\mu\text{A}/V^2, C_{ox}=5f\text{F}/\mu\text{m}^2, C_{ol}=0.2f\text{F}/\mu\text{m}, C=1p\text{F}$$


Assume square-law and ignore the body-effect.

Errors :

- 1-) Settling error

- 2-) Charge injection

- 3-) Overlap cap: C_{gd1}

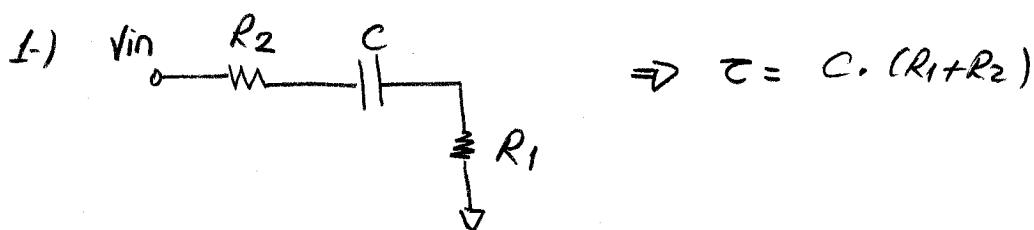

$$R_1 = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 \cdot (3V - V_{TH})} = \frac{1}{200 \frac{\mu\text{A}}{V^2} \cdot 20 \cdot 2V} = 125\Omega$$

$$R_2 = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_2 \cdot (3V - V_S - V_{TH})} = \frac{1}{200 \frac{\mu\text{A}}{V^2} \cdot 20 \cdot 0.5V} = 500\Omega \Rightarrow$$

$$Z = 10\text{ pF} \cdot 625\text{ }\Omega = 6.25\text{ nsec}$$

$$\text{Settling error} = 1.5V \cdot e^{-\frac{ts}{C}} = 1.5 \cdot e^{-\frac{25\text{ ns}}{6.25\text{ ns}}} = 1.5 \times e^{-4} = 1.5 \text{ mV} = 1.5 \text{ mV}_{\parallel}$$

$$= 30 \text{ mV}_{\parallel}$$


2-) Charge injection : Bottom plate sampling \rightarrow we'll consider M_1 only.

$$Q_{ch} = W \cdot L_1 \cdot C_{ox} (V_{gs} - V_{TH})$$

$$= 20 \mu\text{m} \cdot 1 \mu\text{m} \cdot 5 \frac{\text{fF}}{\mu\text{m}^2} \cdot (3 - 1) = 20 \cdot 5 \cdot 2 \text{ fF} \cdot \text{V} \\ = 200 \text{ fF} \cdot \text{V}$$

$$\text{Charge injection error} = \frac{Q_{ch}}{2} \cdot \frac{1}{C} = \frac{200 \text{ fF} \cdot \text{V}}{2} \cdot \frac{1}{10 \text{ pF}} \\ = 10 \text{ mV}_{\parallel}$$

3-) Overlap cap :

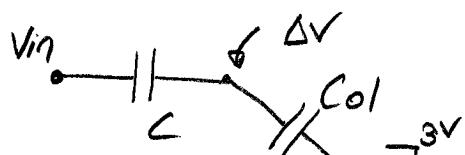

$$\Delta V \cong \frac{Col}{C} \cdot 3 \text{ V}$$

$$Col = C_O \cdot Col = 20 \mu\text{m} \cdot 0.2 \frac{\text{fF}}{\mu\text{m}} = 4 \text{ fF}$$

$$\Delta V = \frac{4 \text{ fF}}{10 \text{ pF}} \cdot 3 \text{ V} = 1.2 \text{ mV}_{\parallel}$$


$$\text{Total sampling error} = -30 \text{ mV} + 10 \text{ mV} + 1.2 \text{ mV}$$

$$= -18.8 \text{ mV}$$




Charge injection and overlap cap increases V_c , while settling error decreases it.

Question 4 (30pts)

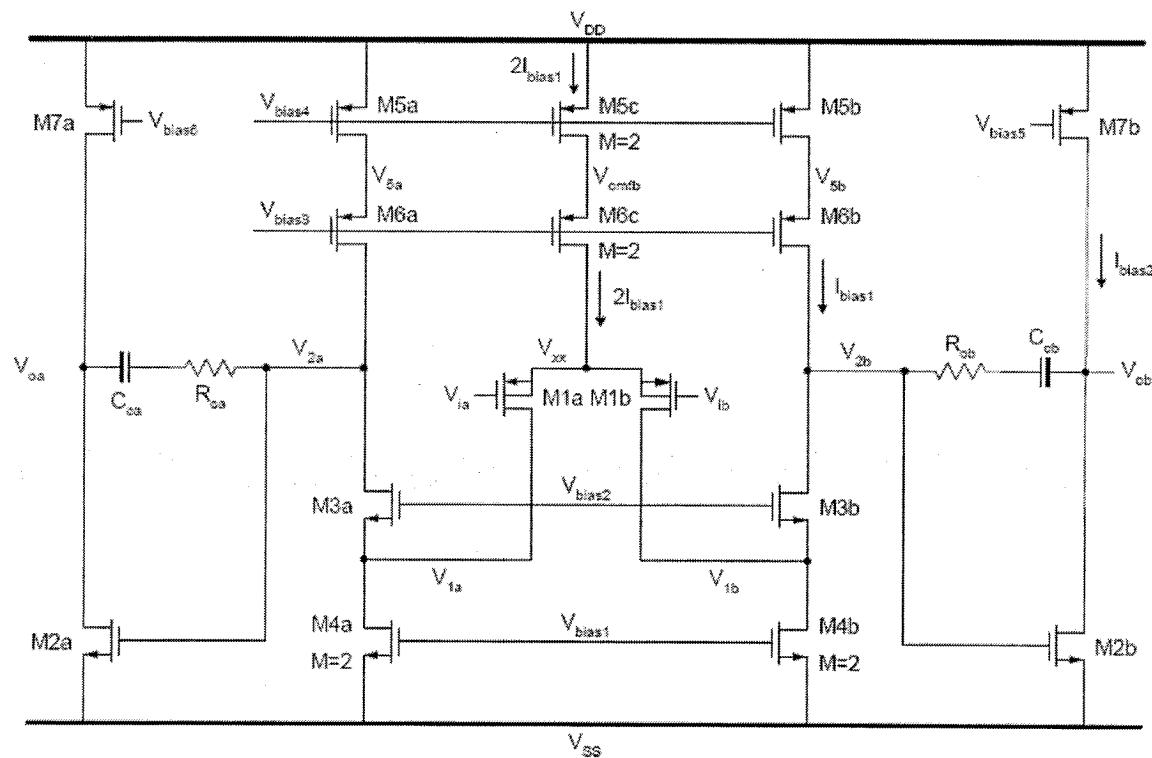

In the OTA above, all channel lengths are the same, all parasitic caps are 0 and $2I_{bias1}=I_{bias2}=I$.

- (10pts)** Calculate the ratio of W_{1a}/W_{2a} that sets the non-dominant pole to of the OTA to 4X the unity gain frequency ω_u of the open loop OTA . You can assume the 2nd pole in the Miller compensation is at $-[gm \text{ of the } 2^{\text{nd}} \text{ stage}]/C_c$.
- (5pts)** Calculate the value of R_{ca} , in terms if the appropriate gm, that sets the RHP zero to infinity.
- (10pts)** Assuming the amplifier is in the feedback loop shown below, estimate the total output voltage noise in terms of V^* 's. For this part you can ignore the effects of the non-dominant pole and the noise from the second stage.

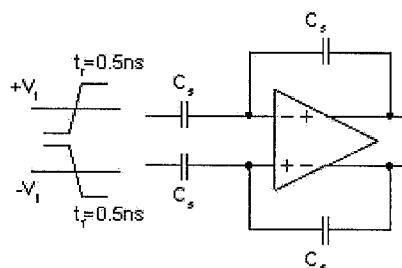

- (5pts)** Using the feedback amplifier in part c, find the slewing time (t_{slew}) when the amplifier is driven by a differential input of $+8V_{1a}^*$.

Q4

a) Miller compensation:

$$\omega_0 \approx \frac{g_{m1a}}{C_c} \quad P_2 = \frac{g_{m2a}}{C_c} \text{ (given)} \quad \frac{g_{m2a}}{C_c} = \frac{g_{m1a}}{C_c} \cdot 4$$

$$\frac{g_{m1a}}{g_{m2a}} = \frac{1}{4}$$

$$g_{m1a} = \sqrt{2 \cdot \left(\frac{\omega}{L}\right)_{1a} \mu_n (ox) I_{D1a}}$$

$$g_{m2a} = \sqrt{2 \cdot \left(\frac{\omega}{L}\right)_{2a} \mu_n (ox) I_{D2a}}$$

$$\frac{g_{m1a}}{g_{m2a}} = \sqrt{\frac{\left(\frac{\omega}{L}\right)_{1a}}{\left(\frac{\omega}{L}\right)_{2a}}} \cdot \frac{I_{D1a}}{I_{D2a}} = \frac{1}{4} \quad I_{D1a} = I/2 \quad I_{D2a} = I \quad L_{1a} = L_{2a}$$

$$\frac{\omega_{1a}}{\omega_{2a}} \cdot \frac{1}{2} = \frac{1}{16} \Rightarrow \frac{\omega_{1a}}{\omega_{2a}} = \frac{1}{8} //$$

b)

$$Z = \frac{g_{m2a}}{C_c} \rightarrow \text{with } R_2 \quad Z = \frac{1}{\left(\frac{1}{g_{m2}} - R_C\right) C_c}$$

$$Z \rightarrow \infty \quad R_C = \frac{1}{g_{m2}} //$$

c)


$$\overline{\frac{V_{reg}}{\Delta f}}^2 = \left(\frac{1}{g_{m1}}\right)^2 \cdot 4kT \gamma (g_{m1} + g_{m4} + g_{m5}) \cdot 2$$

differential

input equivalent noise

In the given feedback configuration $F = \frac{1}{2}$.

$$\left(\overline{\frac{V_{reg}}{\Delta f}}^2 \rightarrow \overline{\frac{V_{od,eq}}{\Delta f}}^2 \right) = \left(\frac{1}{F} \right)^2 \cdot \left| \frac{1}{1 + \frac{s}{\omega_{u,f}}} \right|^2$$

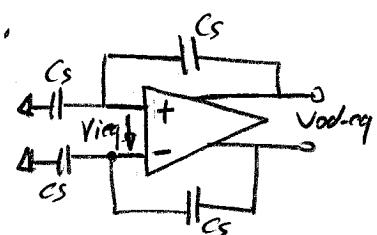

$$\overline{\frac{V_{od,eq}}{\Delta f}}^2 = \underbrace{\left(\frac{1}{g_{m1}} \right)^2 \cdot 4kT \gamma (g_{m1} + g_{m4} + g_{m5}) \cdot 2}_{\overline{\frac{V_{reg}}{\Delta f}}^2} \cdot \underbrace{\left(\frac{1}{F} \right)^2 \left| \frac{1}{1 + \frac{s}{\omega_{u,f}}} \right|^2}_{\left| \frac{V_{od}}{V_{id}} \right|^2} \cdot 10$$

$$\text{Noise integral} = \frac{\omega_{\text{w0}} F}{4} = \frac{1}{4} \frac{g_{m1}}{C_c} \cdot F$$

$$\Rightarrow \overline{V_{\text{od-eq}}^2} = 2 \left(\frac{1}{g_{m1a}} \right)^2 4kT \gamma g_{m1a} \left(1 + \frac{g_{m4a}}{g_{m1a}} + \frac{g_{m5a}}{g_{m1a}} \right) \cdot \left(\frac{1}{F} \right)^2 \cdot \frac{1}{4} \frac{g_{m1a}}{C_c} \cdot F$$

$$\overline{V_{\text{od-eq}}^2} = 2 \cdot \frac{kT}{C_c} \cdot \frac{1}{F} \cdot \gamma \left(1 + \frac{g_{m4a}}{g_{m1a}} + \frac{g_{m5a}}{g_{m1a}} \right)$$

$$g_{m4a} = \frac{2 \cdot I}{V_4^*}$$

$$g_{m1a} = \frac{2 \cdot I/2}{V_4^*}$$


$$\overline{V_{\text{od-eq}}^2} = 2 \cdot \frac{kT}{C_c} \cdot \frac{1}{F} \cdot \gamma \left(1 + 2 \cdot \frac{V_{10}^*}{V_{4a}^*} + \frac{V_{10}^*}{V_{5a}^*} \right)$$

$$\frac{g_{m4a}}{g_{m1a}} = 2 \cdot \frac{V_{10}^*}{V_4^*}$$

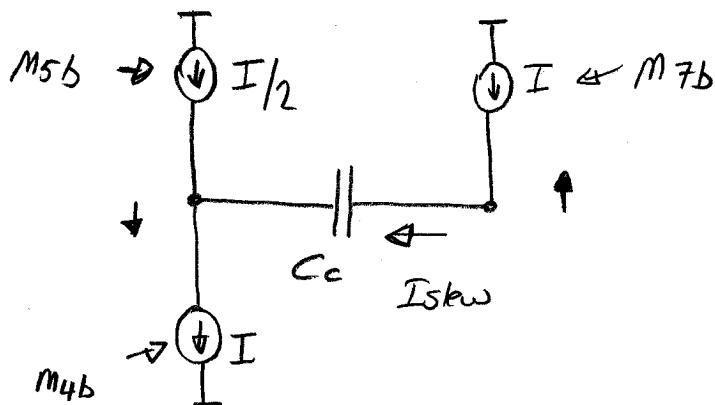d) $\Delta V_{\text{od}} = 8 V_{10}^*$
(Signal gain = 1)

$$\Delta V_{\text{od-linear}} = \frac{V_{10}^*}{F} = 2 V_{10}^* \quad (F = \frac{1}{2})$$

$$\Delta V_{\text{od-slew}} = 6 V_{10}^*$$



I_{slew} is limited by the folded cascode and it is $\frac{I}{2}$


$$\frac{I}{2} \cdot t_{\text{slew}} \cdot \frac{1}{C_c} = 6 \cdot V_{10}^* \Rightarrow t_{\text{slew}} = 6 \cdot C_c \cdot \frac{V_{10}^*}{I/2 - ID_{1a}}$$

$$t_{\text{slew}} = 12 \cdot \frac{C_c}{g_{m1a}}$$

$$t_{\text{slew}} = \frac{12}{\omega_{\text{w0}}} //$$

open loop (not the loop gain)

Question 5 (10pts)

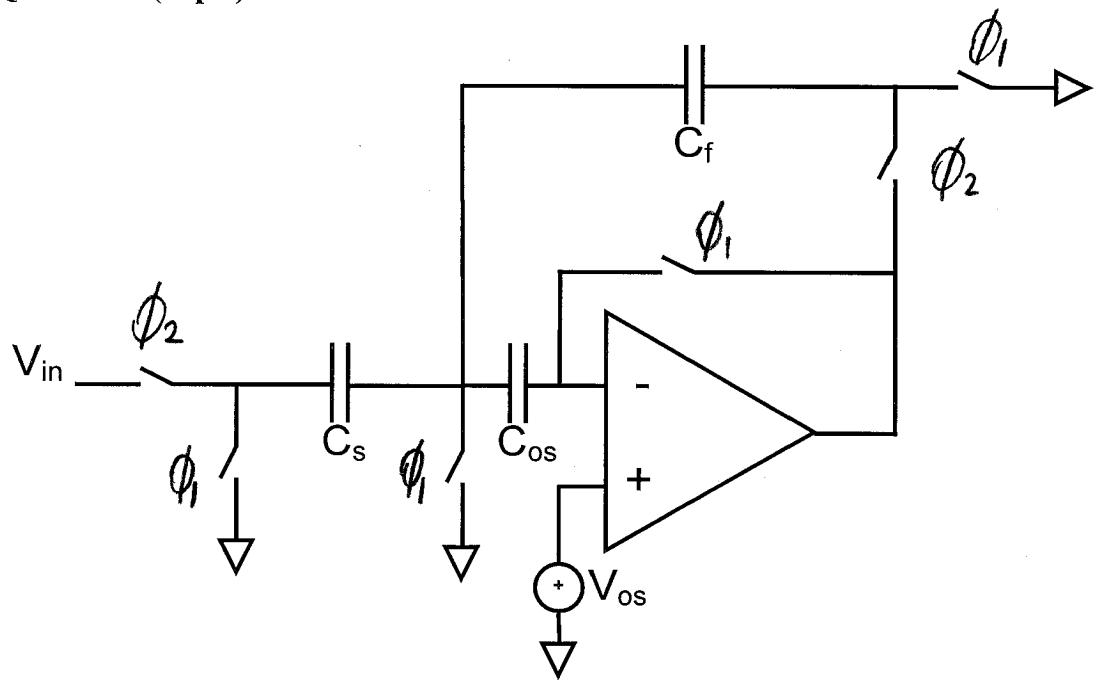

In the switch cap gain circuit above, there are two non-overlapping phases available: Φ_1 , Φ_2 . In order to have an inverting gain stage with offset cancellation, assign appropriate phases (Φ_1 or Φ_2) to switches in the circuit.