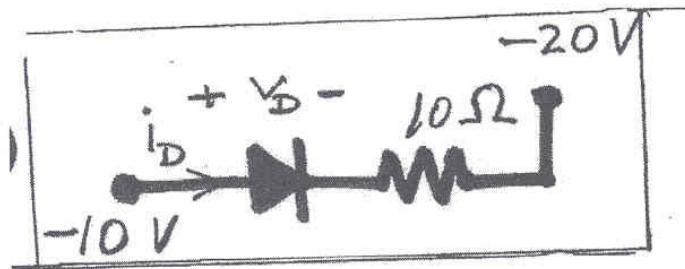


PROBLEM 1 (20 points)

20 / 20

Determine whether the **IDEAL DIODE** in the following two circuits is "ON" or "OFF". You MUST show $i_D > 0$ if diode is "ON", and $v_D < 0$ if diode is "OFF".

(a)



Assume ON

$$i_D = \frac{-10 - (-20)}{10\Omega} = \frac{10}{10\Omega} = 1A$$


$i_D > 0$ SO ASSUMPTION IS CORRECT

$$i_D = \underline{\quad 1A \quad}$$

$$v_D = \underline{\quad 0V \quad}$$

Diode state (ON or OFF): ON

(b)

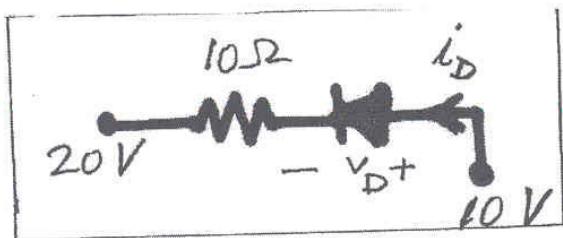

Assume OFF

$$10V - 20V = v_D = -10V$$

$v_D \leq 0$ ✓
ASSUMPTION
IS CORRECT
SINCE $v_D \leq 0$


$$i_D = \underline{\quad 0 \quad}$$

$$v_D = \underline{\quad -10V \quad}$$

Diode state (ON or OFF): OFF

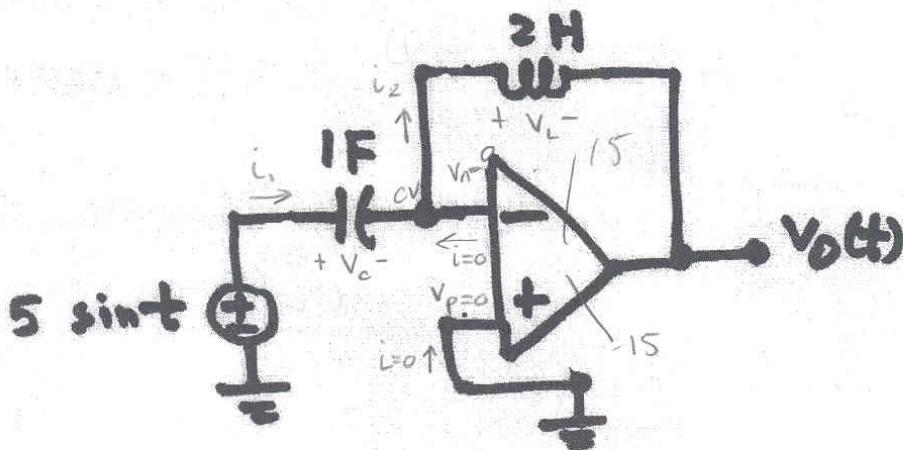PROBLEM 2 (10 points)

Find the output voltage $v_o(t)$ of the following OP AMP circuit. Assume ideal op-amp model with saturation voltage $E_{sat} = \pm 15$ V.



$$\frac{di}{dt}$$

$$\frac{dv}{dt}$$

$$v_c = 5 \sin(t) - 0$$

$$v_c = 5 \sin(t)$$

$$\frac{dv_c}{dt} = 5 \cos(t)$$

$$KCL \Rightarrow i_1 + i_2 = 0$$

$$i_1 = i_2$$

$$i_1 = 1 \cdot 5 \cos(t)$$

$$i_2 = 5 \cos(t) \quad \frac{di_2}{dt} = -5 \sin(t)$$

$$v_L = L(-5 \sin(t))$$

$$v_L = -2(5 \sin(t))$$

$$= -10 \sin(t)$$

10
0

$$0 - (v_o) = v_o(t)$$

$$-(-10 \sin(t)) = v_o(t)$$

$$10 \sin(t) = v_o(t)$$

↓

$$v_o(t) = 10 \sin(t)$$

$$-15 < 10 \sin(t) < 15$$

so IT DOESN'T


RATE SINCE

$v_o(t)_{\text{max}}$ is 10


AND $v_o(t)_{\text{min}} = -10$

PROBLEM 3 (20 points)

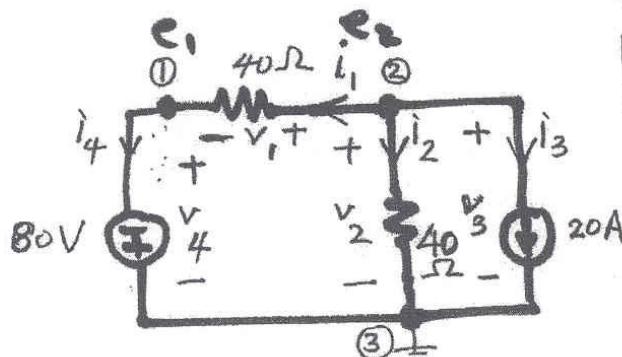(a) Draw the digraph of the following circuit and write down the associated reduced incidence matrix.



DIGRAPH

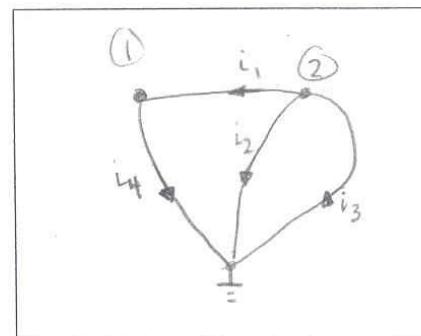

REDUCED INCIDENCE MATRIX: $A = \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$

(b) Write 2 KCL equations and 4 KVL equations directly from the reduced incidence matrix found from part (a).

$$KCL \Rightarrow i_4 - i_1 = 0$$

$$i_1 + i_2 + i_3 = 0$$

$$\begin{bmatrix} -1 & 1 \\ 0 & 1 \\ 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

$$e_2 - e_1 = v_1$$

$$e_2 = v_2$$

$$e_2 = v_3$$

$$e_1 = v_4$$

KCL EQUATIONS:

$i_4 - i_1 = 0$
$i_1 + i_2 + i_3 = 0$


KVL EQUATIONS:

$e_2 - e_1 = v_1$
$e_2 = v_2$
$e_2 = v_3$
$e_1 = v_4$

120

PROBLEM 4 (20 points)

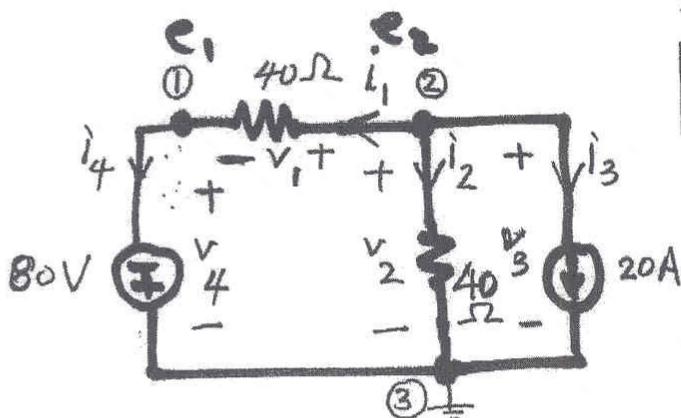- (a) Find the voltage v_2 of the circuit from problem 3 (reproduced below) by applying the SUPERPOSITION theorem.




$$\begin{aligned} e_2 - e_1 &= v_1 = -440 - (-80) = -360 \text{ V} \\ e_2 &= v_2 \quad e_2 = v_2 = v_3 = -440 \text{ V} \\ e_2 &= v_3 \\ e_1 &= v_4 = -80 \text{ V} \\ i_4 &= i_1 \\ i_1 + i_2 + i_3 &= 0 \\ i_3 &= 20 \text{ A} \end{aligned}$$

$$i_2 = \frac{-440 \text{ V}}{40 \Omega} = -11 \text{ A}$$

$$i_1 = -(i_2 + i_3) = -(-11 + 20) = 9 \text{ A}$$

FROM VOLTAGE SOURCE

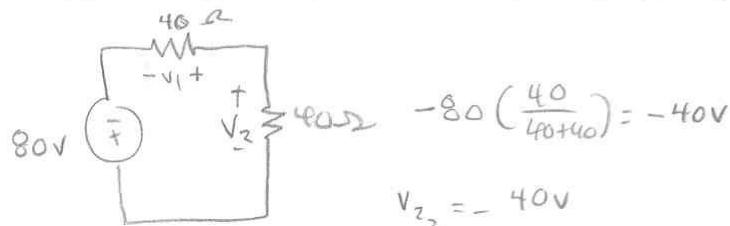

$$-80 \left(\frac{40}{40+40} \right) = -40 \text{ V}$$

$$v_{2_2} = -40 \text{ V}$$


$$80 - v_1 + v_2 = 0$$

$$80 = v_1 - v_2$$

$$40 - (-40) = 80 \checkmark$$

$$v_2 = -400 - 40 = -440 \text{ V}$$

FROM CURRENT SOURCE

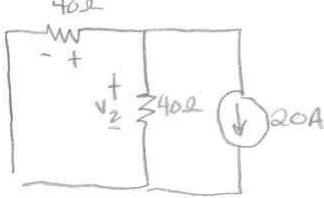

$$20 \left(\frac{40}{40+40} \right) = 10 \text{ A}$$

$$v_{2_1} = -(10)(40) = -400 \text{ V}$$

$$v_2 = -400 \text{ V}$$

$$v_2 = \underline{-440 \text{ V}}$$

- (b) Use your answer from (a) to enumerate the following by inspection:

$v_1 = -360 \text{ V}$, $v_2 = -440 \text{ V}$, $v_3 = -440 \text{ V}$, $v_4 = -80 \text{ V}$	\checkmark
$i_1 = -9 \text{ A}$, $i_2 = -11 \text{ A}$, $i_3 = 20 \text{ A}$, $i_4 = -9 \text{ A}$	

- (c) Validate your solution via Tellegen's Theorem:

$$\sum_i v_i i_i = (-360 \text{ V})(-9 \text{ A}) + (-440 \text{ V})(-11 \text{ A}) + (-440 \text{ V})(20 \text{ A}) + (-80 \text{ V})(-9 \text{ A}) = 0$$



$$3240 + 4840 - 8800 + 720 = 0$$

$$0 = 0 \checkmark$$

PROBLEM 5 (10 points)


- (a) Find the Thevenin equivalent of the following circuit.

THEVENIN EQUIVALENT

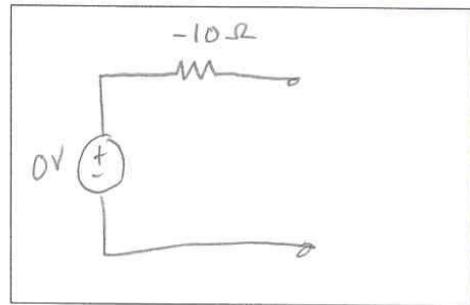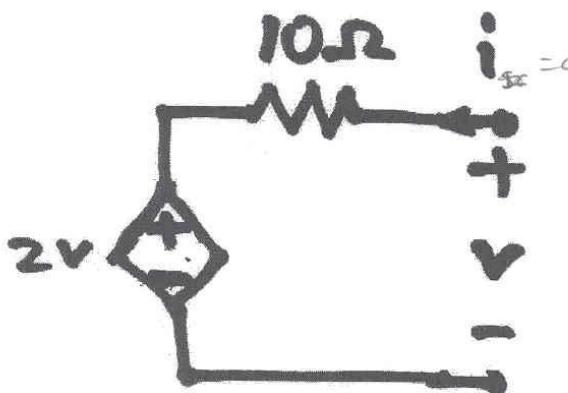

✓

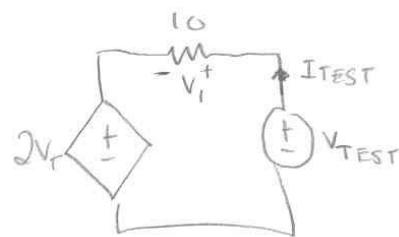$V_{oc} = 0 \}$ SINCE THERE
 $I_{sc} = 0$ ARE NO INDEPENDENT
 FOR VOLTAGE OR CURRENT
 SOURCES



$$R_{eq} = \frac{V_{TEST}}{I_{TEST}}$$


$$R_{eq} = \frac{-10I_{TEST}}{I_{TEST}} = -10\Omega = R_{eq}$$

$$-V_{TEST} + 10I_{TEST} + 2V_{TEST} = 0$$


$$V_{TEST} = -10I_{TEST}$$

- (b) Find the Norton equivalent of the circuit above.

NORTON EQUIVALENT

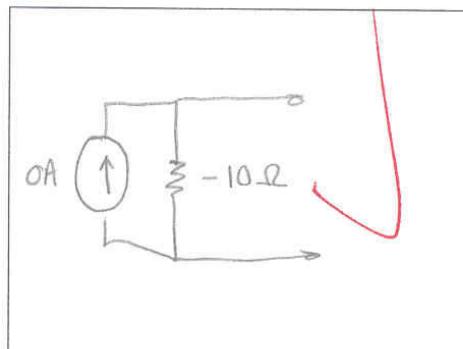


FOR I_{sc}

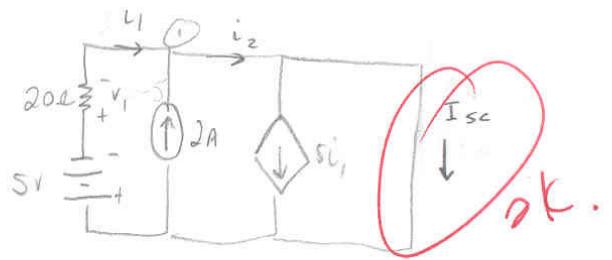

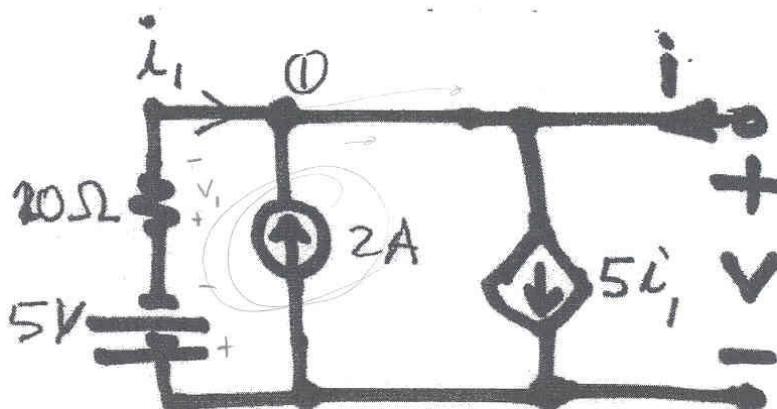PROBLEM 6 (20 points)

For the following circuit:

- Find the open-circuit voltage v_{oc} by assuming $i = 0$.
- Find the short-circuit current i_{sc} by assuming $v = 0$.
- Find the Thevenin equivalent circuit from (a) and (b).



For v_{oc}

$$kcl @ \textcircled{1} \quad i_1 + 2 = 5i_1$$


$$2 = 4i_1 \\ i_1 = \frac{1}{2}A$$

$$kvl \quad -v_{oc} - v_1 - 5 = 0$$

$$v_1 = (\frac{1}{2})(20) - 5 = -15V = v_{oc}$$

$$R_{eq} = \frac{v_{oc}}{i_{sc}} = \frac{-15V}{3A} = -5\Omega$$

20

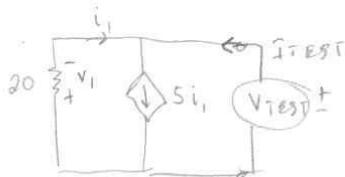

$$R_{eq} = \frac{V_{TEST}}{I_{TEST}}$$

$$i_1 + I_T = 5i_1$$

$$I_T = 4i$$

$$-V_{TEST} = 20i$$

$$V_T = -20i$$

$$R_{eq} = \frac{-20i}{4i} = -5\Omega = R_{eq}$$

$$\text{(a)} \quad v_{oc} = -15V$$

$$\text{(b)} \quad i_{sc} = 3A$$

THEVENIN EQUIVALENT CIRCUIT

